
THE GEORGE WASHINGTON UNIVERSITY

WASHINGTON, DC

SCHOOL OF ENGINEERING AND APPLIED SCIENCE
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING
ECE 2110: CIRCUIT THEORY LABORATORY

Experiment #5:
Thévenin's Theorem, Mesh Current, and Node Voltage Analysis

EQUIPMENT

<i>Lab Equipment</i>	<i>Equipment Description</i>
(1) DC Power Supply	Supplied by the AD2
(1) Digital Multimeter (DMM)	Handheld Model
(1) Breadboard	Prototype Breadboard
(3) Test Leads	Banana to Alligator Lead Set

Table 1 – Equipment List

COMPONENTS

<i>Type</i>	<i>Value</i>	<i>Symbol Name</i>	<i>Multisim Part</i>	<i>Description</i>
Resistor	750 Ω	R ₁	Basic/Resistor	---
Resistor	1k Ω	R ₂	Basic/Resistor	---
Resistor	1.5k Ω	R ₃	Basic/Resistor	---
Resistor	3k Ω	R ₄	Basic/Resistor	---
Resistor	4k Ω	R ₅	Basic/Resistor	---
Resistor	10k Ω	R ₆	Basic/Resistor	---
Resistor	12k Ω	R ₇	Basic/Resistor	---
Resistor	15k Ω	R ₈	Basic/Resistor	---

Table 2 – Component List

OBJECTIVES

- To understand Thévenin's theorem of equivalent circuits
- To analyze and reduce three DC circuits to their Thévenin equivalent circuits by hand
- To analyze and reduce three DC circuits to their Thévenin equivalent circuits with Multisim
- To analyze and reduce three DC circuits to their Thévenin equivalent circuits in lab

INTRODUCTION

In this lab, you must find the Thévenin and Norton equivalents for three separate circuits. You will first perform the analysis by hand using the techniques that you have learned in lecture and in your homework. Then, you will simulate the circuits in Multisim, using it to find the Thévenin and Norton equivalents. Finally, you will build the three circuits in lab and measure them to find the Thévenin and Norton equivalents. In your lab report, you will compare and analyze the results from each technique.

Thévenin's Theorem

Thévenin's Theorem for DC circuits states that any two port linear network may be replaced by a single voltage source with an appropriate internal resistance. The Thévenin equivalent will produce the same load current and voltage as the original circuit to any load. Consequently, if many different loads or sub-circuits are under consideration, using a Thévenin equivalent usually proves to be a much quicker method of analysis. Any complex circuit consisting of multiple sources and components can be reduced to a single voltage source, the Thévenin voltage, in series with its internal resistance, the Thévenin resistance.

The **Thévenin voltage**, V_{TH} , is found by determining the open-circuit output voltage. The **Thévenin resistance**, R_{TH} , is found by replacing any DC sources with their internal resistances and determining the resulting combined resistance as seen from the two ports using standard series-parallel analysis techniques. A voltage source would be replaced by a short, zero resistance, and a current source would be replaced by an open, infinite resistance. In the laboratory, the Thévenin resistance may be found using an ohmmeter (again, replacing the sources with their internal resistances) or by using the matched load technique. The matched load technique involves replacing the load with a variable resistance and then adjusting it until the load voltage is precisely one-half of the unloaded voltage. This would imply that the other half of the voltage must be dropped across the equivalent Thévenin resistance, and as the Thévenin circuit is a simple series loop then the two resistances must be equal as they have identical currents and voltages.

Norton's Theorem

Norton's Theorem for DC circuits states that any two port linear network may be replaced by a single current source with an appropriate internal resistance in parallel. It is closely related to Thévenin's Theorem, and either simplified representation works equally well. Any complex circuit consisting of multiple sources and components can be reduced to a single current source, the Norton or short-circuit current, in parallel with its internal resistance, which is the same as the Thévenin resistance.

The **Norton current** is found by determining the short-circuit output current, I_{SC} . The internal resistance can be determined in the same manner as was explained above for the Thévenin resistance.

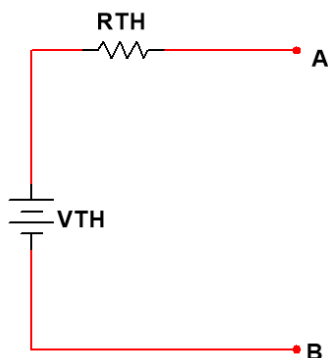


Figure 1 – Thévenin Equivalent Circuit

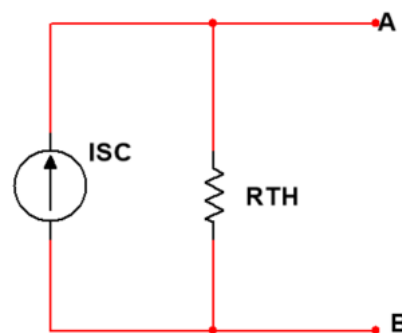


Figure 2 – Norton Equivalent Circuit

Mesh Current Analysis

Multi-source DC circuits may be analyzed using a mesh current technique. The process involves identifying a minimum number of small loops such that every component exists in at least one loop. **Kirchhoff's Voltage Law** is then applied to each loop, meaning that the algebraic sum of the voltages around each loop must equal zero. The loop currents are referred to as mesh currents as each current interlocks or meshes with the surrounding loop currents. As a result, there will be a set of simultaneous equations created, an unknown mesh current for each loop. Once the mesh currents are determined, various branch currents and component voltages may be derived.

Node Voltage Analysis

Multi-source DC circuits may be analyzed using a node voltage technique. The process involves identifying all of the circuit nodes, a node being a point where various branch currents combine. A reference node, usually ground, is included. **Kirchhoff's Current Law** is then applied to each node, meaning that the algebraic sum of the currents into and out of each node must equal zero. Consequently, a set of simultaneous equations are created with an unknown voltage for each node with the exception of the reference. In other words, a circuit with a total of five nodes including the reference will yield four unknown node voltages and four equations. Once the node voltages are determined, various branch currents and component voltages may be derived.

How to Use All Three DC Voltage Outputs

For Part II of this lab, you will need to build a circuit that has three separate voltage sources. It is very important that you know how to properly utilize the AD2 so that you can create this complex circuit.

Remember that the AD2 can supply anywhere between -5V to 5V. The AD2 can produce DC voltage through the "Supplies" tab and the "Wavegen" tab. Within the Wavegen tab, you just need to set the "type" to DC, and then change the offset to whatever voltage you need. **The play button for the Wavegen tab does not control it in this case.** Above the "Type" selection box is a white check box that says "enable". This box is what turns the DC Wavegen on and off. The different voltage sources within the AD2 and its adapter all share a common ground. If the negative sides of the voltage sources are grounded in your schematic, they need to be tied together to the same ground. To do this, make sure to connect the bottoms (the ground wire) of the voltage sources onto the same ground rail. Without the adapter, the ground wires are the black wires coming from the pins with the down arrows, which are third from the left. An example of this is shown below.

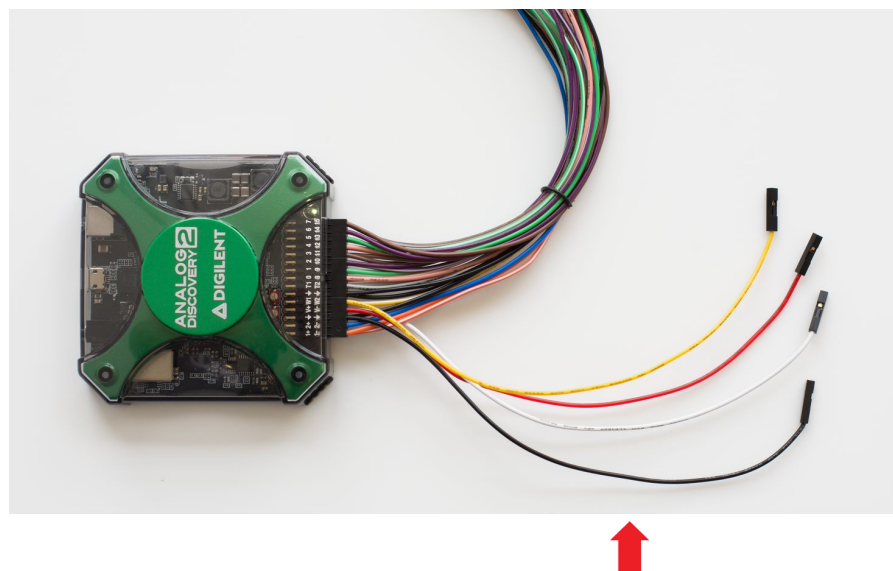


Figure 3 - AD2 Power Supply Connections

PRELAB

This prelab consists of three circuits to be reduced using Thévenin's Theorem. You are required to complete both hand calculations and Multisim simulations before coming to lab. **This prelab requires more analysis than previous labs; please allocate the proper amount of time to complete it early on.**

Part I – Circuit #1 Analysis

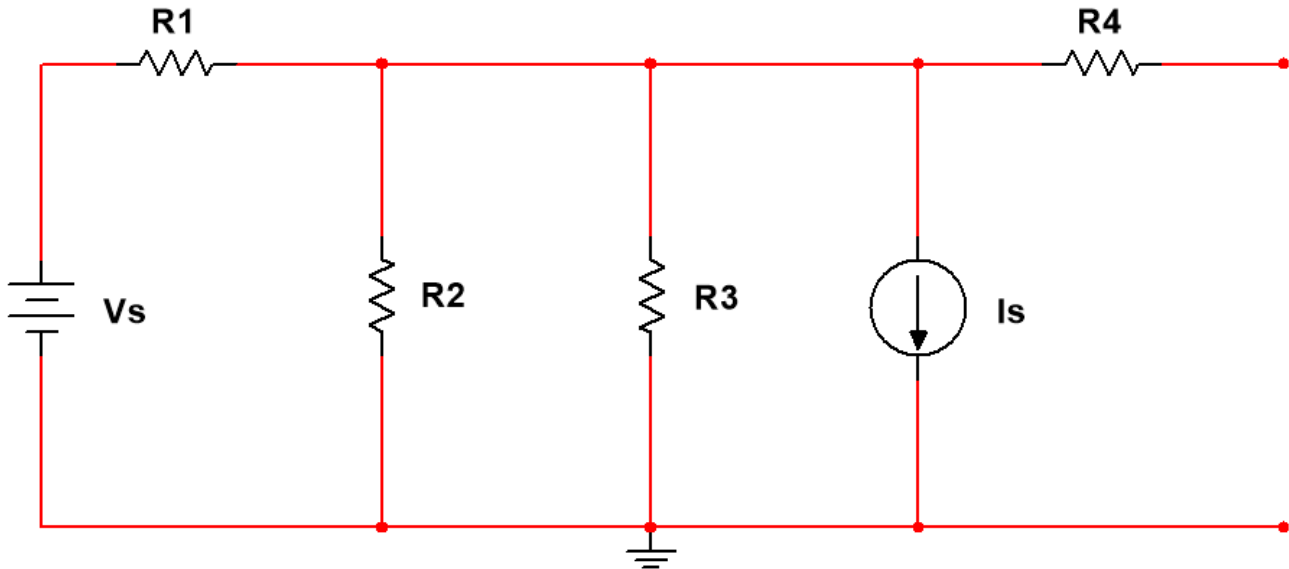


Figure P.1.1 – Circuit #1

In Figure P.1.1, the voltage source $V_s = 5V$ and the current source $I_s = 2\text{ mA}$.

1. Calculate the following from the perspective of terminals A and B. **Show all work.**
 - a. Thévenin voltage (V_{TH})
 - b. Thévenin resistance (R_{TH})
 - c. Norton current, also called the short-circuit current (I_{SC})
2. Use your results to fill in the appropriate values for Figure P.1.2 and Figure P.1.3 below:

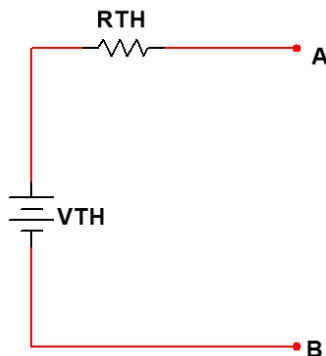


Figure P.1.2 – Thévenin Equivalent of Circuit #1

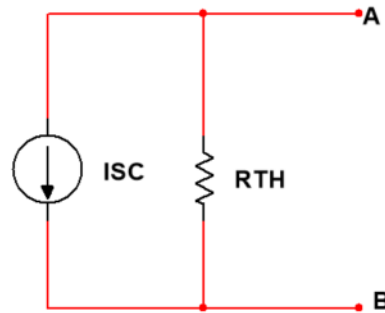


Figure P.1.3 – Norton Equivalent of Circuit #1

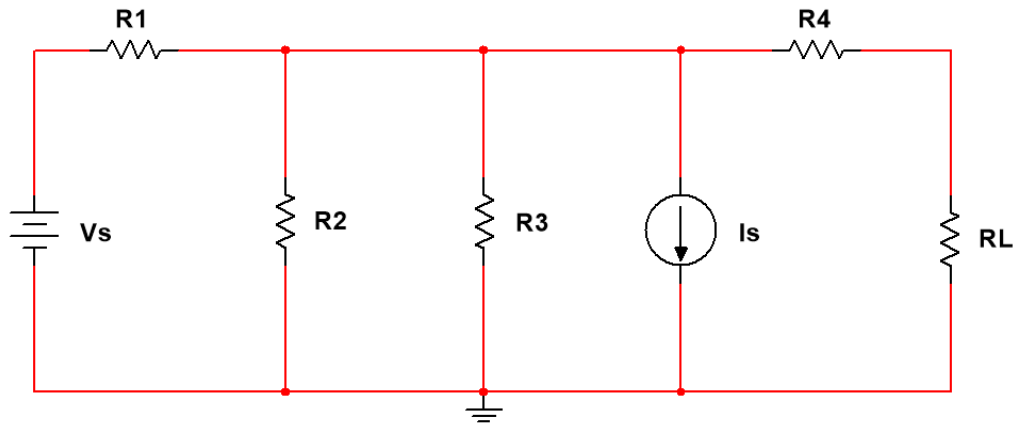


Figure P.1.4 – Circuit #1 with Load Resistor Attached

- Calculate the voltage across and current through R_L for the circuit in Figure P.1.4, which has a $1\text{k}\Omega$ load resistor R_L attached across terminals A and B.

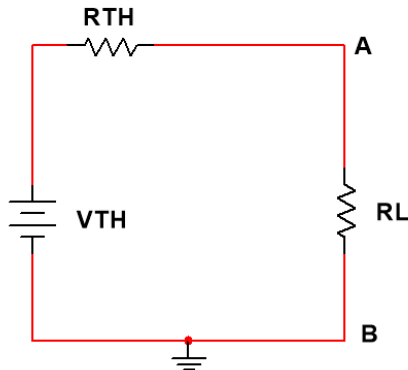


Figure P.1.5 – Thévenin Equivalent with Load Resistor

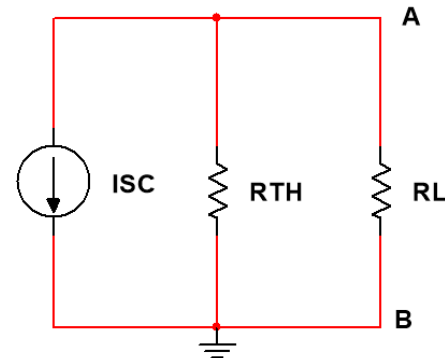


Figure P.1.6 – Norton Equivalent with Load Resistor

- Calculate the voltage across and current through R_L for these circuits, which have a $1\text{k}\Omega$ load resistor R_L attached across terminals A and B.
- Simulate the circuit from Figure P.1.1 in Multisim:
 - Use the tutorial on the lab website (**Multisim Tutorial #2: Using Multisim to find V_{TH} , I_{SC} , R_{TH}**) to learn how to find V_{TH} , I_{SC} , and R_{TH} for a circuit in Multisim.
 - Build the circuit in Figure P.1.1 in Multisim and find its V_{TH} , I_{SC} , and R_{TH} .
 - Build the equivalent circuits in Figure P.1.2 and Figure P.1.3 in Multisim.
 - In Multisim, attach a $1\text{k}\Omega$ load resistor (R_L) to the circuit as you did in Figure P.1.4. Measure and record the simulated voltage across and current through R_L .
 - In Multisim, attach $1\text{k}\Omega$ load resistors (R_L) to the equivalent circuits in Figure P.1.5 and Figure P.1.6. Measure and record the simulated voltage across and current through R_L .

Electrical Quantity	V_{TH}	R_{TH}	I_{SC}	Original Circuit		Equivalent Circuit	
				V_{RL}	I_{RL}	V_{RL}	I_{RL}
Calculated							
Simulated							
Percent Error							

Table P.1 – Circuit #1 Data

Part I – Circuit #1 Analysis Continued

6. Now **Simulate** the circuit shown in **Figure P.1.7**, which replaces the current source with a voltage source (V2). The value of V2 is set at 1.44V.
 - a. **Measure** the voltage and current across point A* and B*. What do you notice about these values compared to those in **Table P.1**?
 - b. Now **Insert** RL into this circuit, shown in **Figure P.1.8**. Measure the current going through and the voltage across RL. What do you notice about these values compared to those in **Table P.1**?

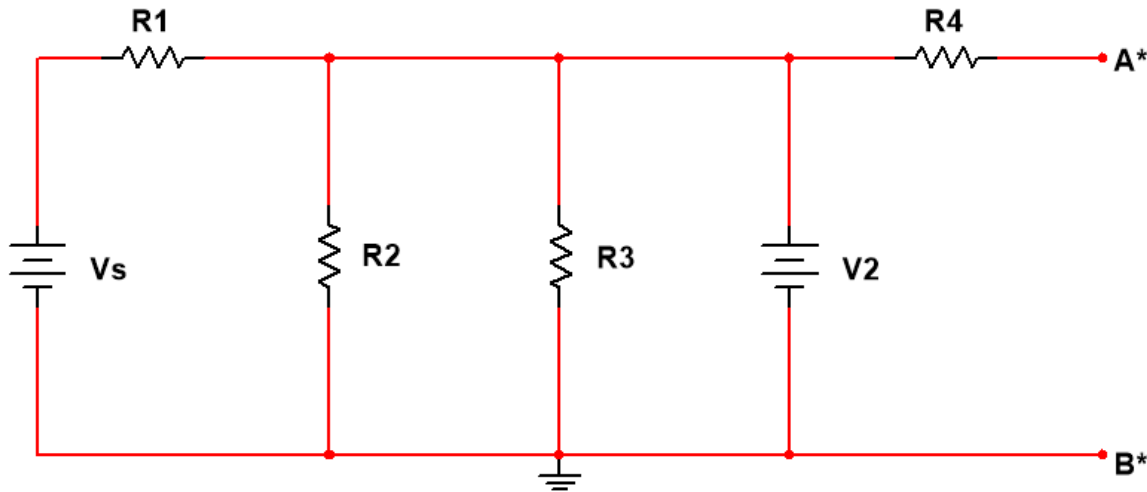


Figure P.1.7

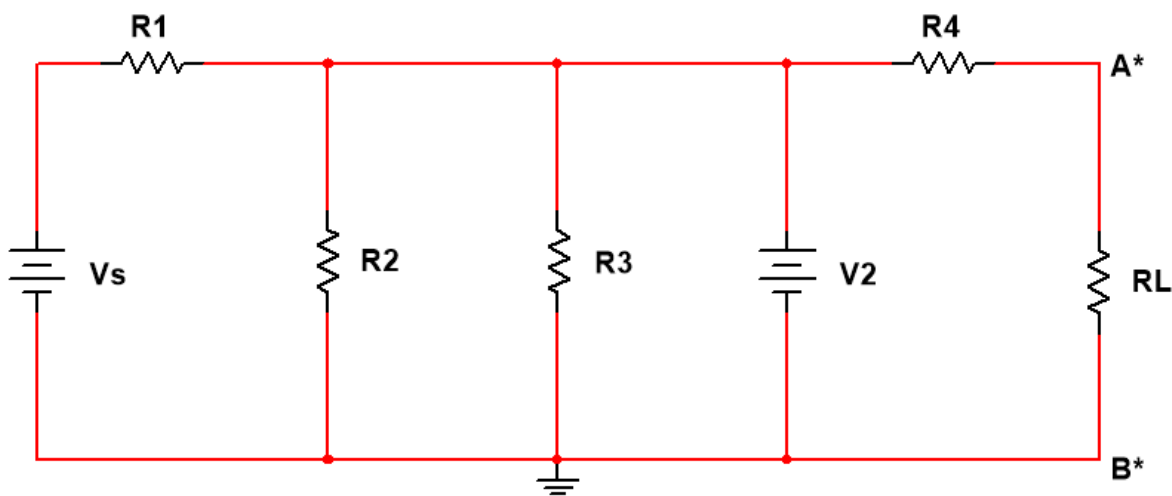


Figure P.1.8

Part II – Circuit #2 Analysis

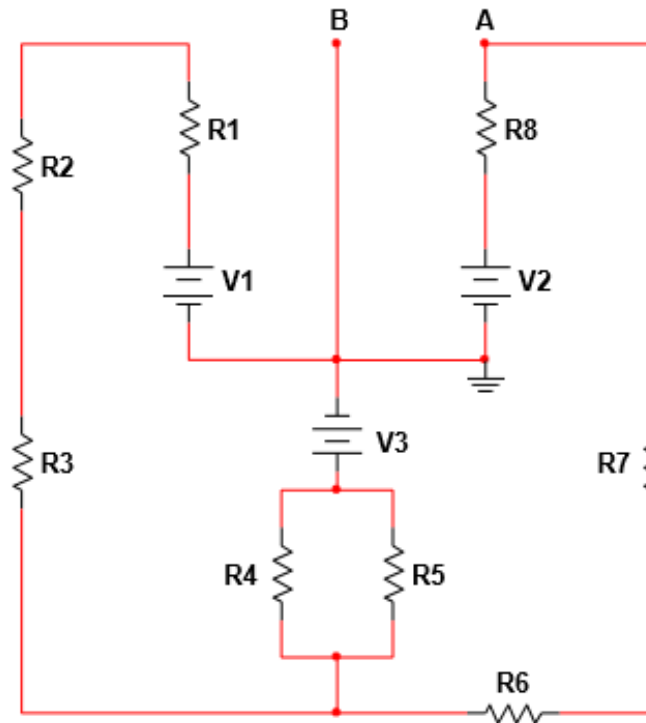


Figure P.2.1 – Circuit #2

In **Figure P.2.1**, the voltage sources **V1 = 3V**, **V2 = 5V**, and **V3 = -5V**.

1. **Calculate** the following from the perspective of terminals A and B. **Show all work.**
 - a. Thévenin voltage (V_{TH})
 - b. Thévenin resistance (R_{TH})
 - c. Norton current, also called the short-circuit current (I_{sc})
2. **Use** your results to fill in the appropriate values and draw the **Thévenin** and **Norton equivalents** as you did in Part I.
3. **Attach** a 1k Ω load resistor R_L across terminals A and B in **Figure P.2.1** and **calculate** the **voltage across** and **current through R_L** for the new circuit.
4. **Attach** a 1k Ω load resistor R_L across terminals A and B in the equivalent circuits that you drew and **calculate** the **voltage across** and **current through R_L** for the new circuits.
6. **Simulate** the circuit from **Figure P.2.1** in Multisim:
 - a. **Build** the circuit in **Figure P.2.1** in Multisim and find its V_{TH} , I_{sc} , and R_{TH} .
 - b. **Build** the equivalent circuits in Multisim.
 - c. In Multisim, attach a 1k Ω load resistor (R_L) to the original circuit. **Measure** and **record** the simulated voltage across and current through R_L .
 - d. In Multisim, attach 1k Ω load resistors (R_L) to the equivalent circuits. **Measure** and **record** the simulated voltage across and current through R_L .

Electrical Quantity	V_{TH}	R_{TH}	I_{sc}	Original Circuit		Equivalent Circuit	
				V_{RL}	I_{RL}	V_{RL}	I_{RL}
Calculated							
Simulated							
Percent Error							

Table P.2 – Circuit #2 Data

Part III – Circuit #3 Analysis

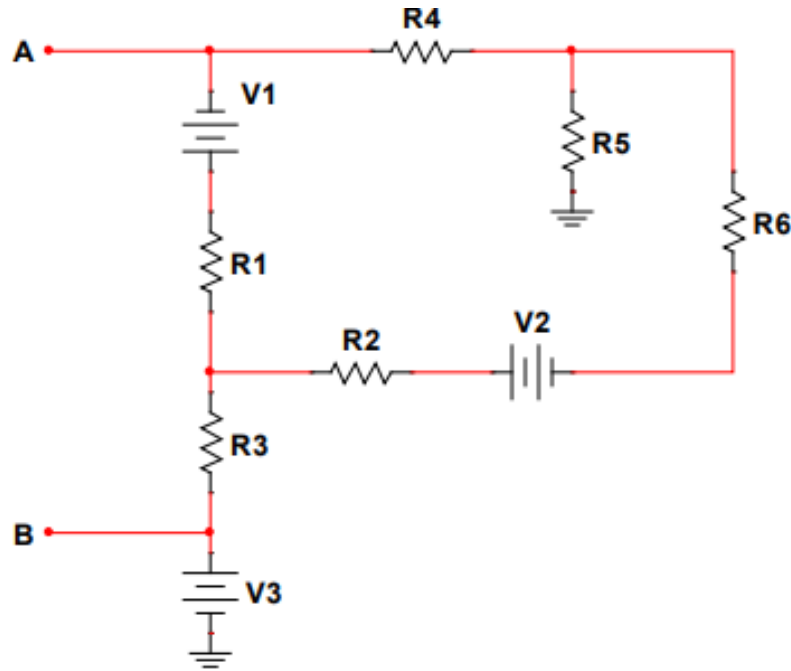


Figure P.3.1 – Circuit #3

In **Figure P.3.1**, the voltage sources **V1 = 3V**, **V2 = 6V**, and **V3 = 9V**.

1. **Calculate** the following from the perspective of terminals A and B. **Show all work.**
 - a. Thévenin voltage (V_{TH})
 - b. Thévenin resistance (R_{TH})
 - c. Norton current, also called the short-circuit current (I_{SC})
2. **Use** your results to fill in the appropriate values and draw the **Thévenin** and **Norton equivalents** as you did in Part I and Part II.
3. **Attach** a $1k\Omega$ load resistor R_L across terminals A and B in **Figure P.3.1** and **calculate** the **voltage across** and **current through R_L** for the new circuit.
4. **Attach** a $1k\Omega$ load resistor R_L across terminals A and B in the equivalent circuits that you drew and **calculate** the **voltage across** and **current through R_L** for the new circuits.
7. **Simulate** the circuit from **Figure P.3.1** in Multisim:
 - a. **Build** the circuit in **Figure P.3.1** in Multisim and find its V_{TH} , I_{SC} , and R_{TH} .
 - b. **Build** the equivalent circuits in Multisim.
 - c. In Multisim, attach a $1k\Omega$ load resistor (R_L) to the original circuit. **Measure** and **record** the simulated voltage across and current through R_L .
 - d. In Multisim, attach $1k\Omega$ load resistors (R_L) to the equivalent circuits. **Measure** and **record** the simulated voltage across and current through R_L .

Electrical Quantity	V_{TH}	R_{TH}	I_{SC}	Original Circuit		Equivalent Circuit	
				V_{RL}	I_{RL}	V_{RL}	I_{RL}
Calculated							
Simulated							
Percent Error							

Table P.3 – Circuit #3 Data

LAB

Part I – Circuit #1 Measurements

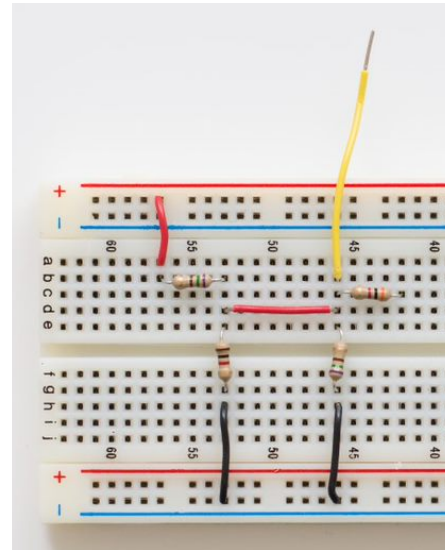
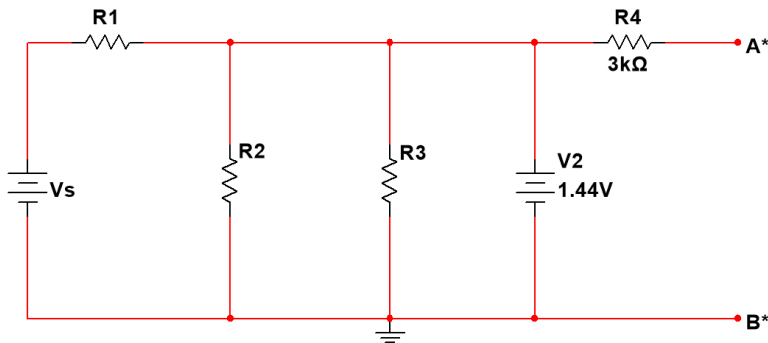


Figure 1.1 – Circuit #1

1. **Build** the circuit from **Part I** of the prelab shown again in **Figure 1.1** on a breadboard. Make sure you have WaveForms open and your AD2 is connected to it. For this circuit, it is recommended that you use the DC portion of the “Wavegen” as V2.
2. **Measure** the circuit to find V_{TH} , R_{TH} , and I_{SC} .
 - a. **V_{TH} Measurement:** Use the DMM to measure the **voltage** between terminals A* and B*.
 - b. **I_{SC} Measurement:** Switch the DMM to current mode and **measure the current between** terminals A* and B*.

Note: Remember that the DMM in current mode has a very small internal resistance, such that connecting it directly between terminals A and B* short-circuits A* to B*. This easily gives us the short-circuit current in this case.*
 - c. **R_{TH} Measurement:**
 - i. **Turn off** and **remove** the DC power supply connections used for Vs and Vs2.
 - ii. **Use** wires to connect where both voltage sources Vs and Vs2 originally were in your circuit.

*Note: As discussed in the Introduction, we must “short” the voltage sources. In real life, however, we cannot simply short the power supply as it would overload it. ***You absolutely must remove the power supply before shorting it.****
 - iii. **Measure** the **resistance** between terminals A* and B* using the DMM.
3. **Remove** the wires used to short the voltage sources and **reconnect** the AD2 to the circuit.
4. **Connect** a 1kΩ load resistor R_L to terminals A* and B* and **measure the voltage across** and the **current through** R_L .
5. **Build** the **Thévenin Equivalent** circuit from **Figure P.1.5** with the load R_L attached.
 - a. **Set** the AD2's output to V_{TH} .
 - b. **Measure** the **voltage across** and the **current through** R_L .
6. **Connect** a resistor between terminals A* and B* that is **equal** to the **Thévenin resistance** (R_{TH}) you calculated. **Measure** the **voltage across** (V_{RTH}) and the **current through** (I_{RTH}) the resistor.
7. **Record** all measured data in the **Table 1.1** and **calculate** the **percent error** between your simulated and measured results.

Electrical Quantity	V_{TH}	R_{TH}	I_{SC}	V_{RTH}	I_{RTH}	Original		Equivalent	
						V_{RL}	I_{RL}	V_{RL}	I_{RL}
Calculated									
Simulated									
Measured									
Percent Error									

Table 1.1 – Circuit #1 Data

Part II – Circuit #2 Measurements

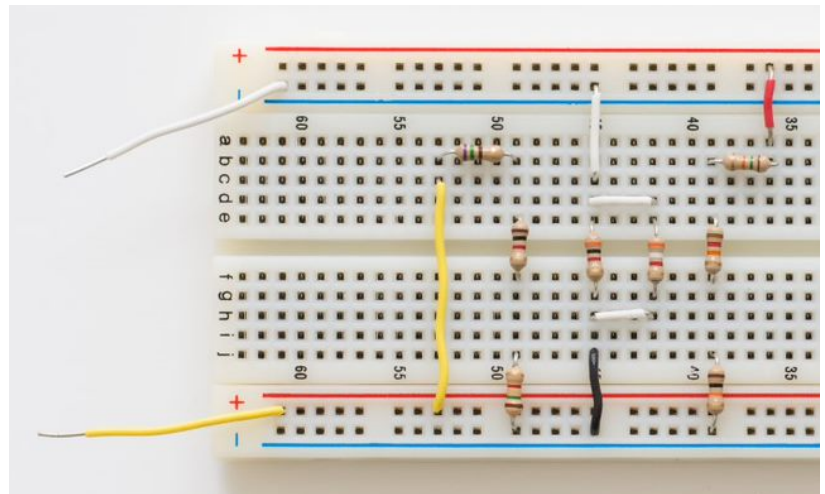
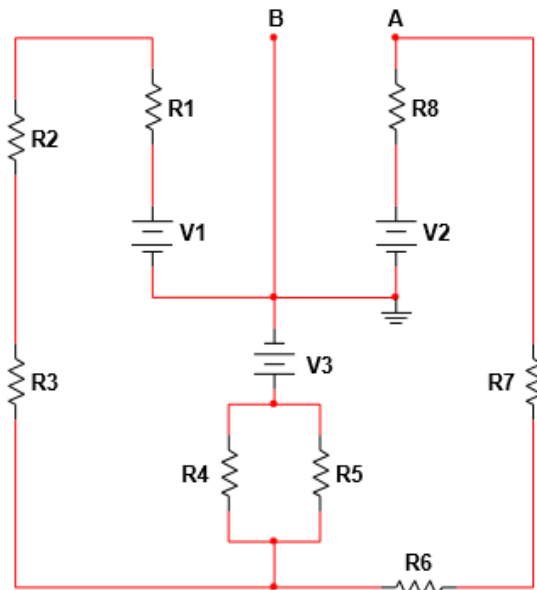


Figure 2.1 – Circuit #2

1. **Build** the circuit from **Part II** of the prelab shown again in **Figure 2.1** on a breadboard.
 - a. Refer to the **Introduction** to recall how to set up your circuit and AD2 with three voltage sources. It's recommended that you use the "Wavegen" for V1, and then use "Supplies" for V2 and V3.
2. **Measure** the circuit to find **V_{TH}**, **R_{TH}**, and **I_{SC}**.
 - a. **V_{TH} Measurement:** Use the **DMM** to measure the **voltage** between terminals A and B. Make sure in WaveForms both the "Supplies" voltages are set to +5V and -5V respectively, and that the "Wavegen" is set to DC and 3V Offset. Hit the play button on both tabs to turn them on.
 - b. **I_{SC} Measurement:** **Switch** the DMM to current mode and **measure** the **current** between terminals A and B.
 - c. **R_{TH} Measurement:**
 - i. **Turn off** and **remove** the DC power supply connections used for V_s and I_s.
 - ii. **Use** a wire to connect where the voltage source V_s originally was in your circuit.
 - iii. **Open** the location where I_s originally was in your circuit.
 - iv. **Measure** the **resistance** between terminals A and B using the DMM.
3. **Remove** the wire used to short the voltage source and **reconnect** the power supplies to the circuit.
4. **Connect** a 1kΩ load resistor R_L between terminals A and B and **measure** the **voltage across** and the **current through** R_L.
5. **Build** the **Thévenin Equivalent** as you did for Circuit #1.
 - a. **Set** the power supply to **V_{TH}**.
 - b. **Measure** the **voltage across** and the **current through** R_L.
6. **Connect** a resistor between terminals A and B that is **equal** to the **Thévenin resistance** (R_{TH}) you calculated. **Measure** the **voltage across** (V_{RTH}) and the **current through** (I_{RTH}) the resistor.
7. **Record** all measured data in the **Table 2.1** and **calculate** the **percent error** between your simulated and measured results.

Electrical Quantity	V _{TH}	R _{TH}	I _{SC}	V _{RTH}	I _{RTH}	Original		Equivalent	
						V _{RL}	I _{RL}	V _{RL}	I _{RL}
Calculated									
Simulated									
Measured									
Percent Error									

Table 2.1 – Circuit #1 Data

Part III – Thévenin Design Problem

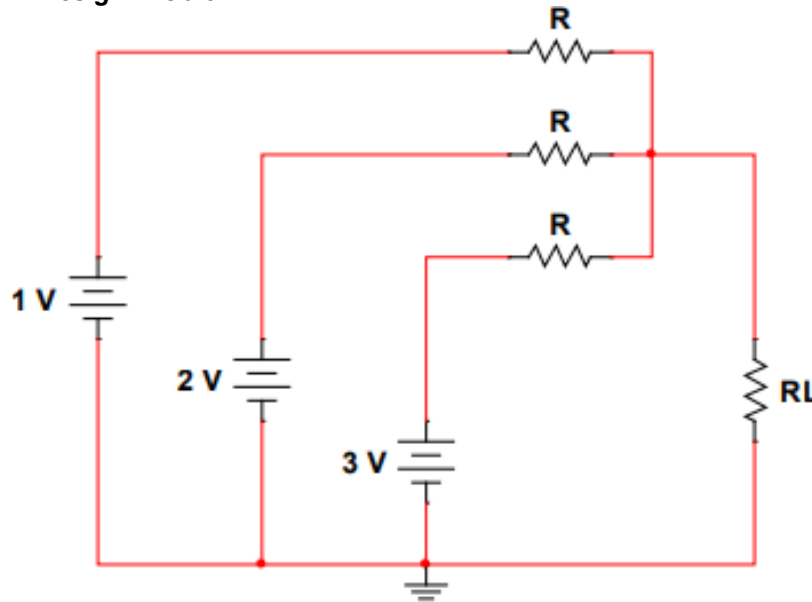


Figure 3.1 – Design Problem

1. **Determine** the resistances R and R_L such that the following specifications are met:
 - **Voltage across** R_L is equal to $\frac{1}{2}V_{TH}$
 - **Maximum power** dissipated by R_L is 3mW

***Hint:** Start by removing the load resistor and finding the Thévenin equivalent circuit as you have done for the previous circuits in this lab. You will need to find the value for R_L before solving for R . Also, note that all three resistors labeled R are the same value resistance.*

2. For your circuit with the calculated value of R , is there any other resistor that could be substituted in for R_L to increase the power dissipated by the load? **Explain.**

POST-LAB ANALYSIS

Include answers to the following questions in the Analysis and Discussion section of your lab report.

1. When you attach the $1\text{k}\Omega$ load resistor (R_L) to any of the circuits in the lab, is the voltage across R_L equal to V_{TH} ? Is the current through R_L equal to I_{SC} ?
2. Is there any load resistor (R_L) that you could attach to the circuit to achieve both V_{TH} and I_{SC} at the same time? Explain.
3. When you attach the Thévenin equivalent resistance (R_{TH}) to any of the circuits in the lab, is there a relationship between V_{TH} and $V_{R_{TH}}$? What about I_{SC} and $I_{R_{TH}}$?

Include the following in the Conclusion of your lab report:

1. Discuss how Thévenin's Theorem helps you simplify the circuit analysis. For example, consider this idea when writing your conclusion: is it easier to use the Thevenin equivalent circuit to determine the voltage across and current through the load resistor (R_L) or is it easier to use the original circuit?
2. What is the purpose of the Thévenin Equivalent circuit?