

---

# THE GEORGE WASHINGTON UNIVERSITY

---

WASHINGTON, DC

**SCHOOL OF ENGINEERING AND APPLIED SCIENCE  
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING  
ECE 2110: CIRCUIT THEORY LABORATORY**

**Experiment #6:  
Maximum Power Transfer Theory Applied to Lab Equipment**

## **EQUIPMENT**

<b>Lab Equipment</b>	<b>Equipment Description</b>
(1) DC Power Supply	Supplied by the AD2 and KLY-2402000
(1) Digital Multimeter (DMM)	Handheld Model
(1) Breadboard	Prototype Breadboard
(3) Test Leads	Banana to Alligator Lead Set
(1) AA Battery	Standard AA 1.5V Battery

Table 1 – Equipment List

## **COMPONENTS**

<b>Type</b>	<b>Value</b>	<b>Symbol Name</b>	<b>Multisim Part</b>	<b>Description</b>
Resistor	750 $\Omega$	R <sub>p</sub>	Basic/Resistor	---
Resistor	3.3M $\Omega$	R <sub>1</sub> (Part I)	Basic/Resistor	---
Resistor	9.1M $\Omega$	R <sub>1</sub> (Part IV)	Basic/Resistor	---
Resistor	270k $\Omega$	R <sub>2</sub>	Basic/Resistor	---
Resistor	10k $\Omega$	R <sub>3</sub>	Basic/Resistor	---
Resistor	3.3k $\Omega$	R <sub>4</sub>	Basic/Resistor	---
Resistor	1k $\Omega$	R <sub>5</sub>	Basic/Resistor	---
Resistor	680 $\Omega$	R <sub>6</sub>	Basic/Resistor	---

Table 2 – Component List

## **OBJECTIVES**

- Use maximum power transfer theory to measure the internal resistances of a DMM
- Use Thevenin theory to determine internal resistances of a DC battery and the KLY 2402000.
- Learn how to use maximum power transfer theory to determine internal resistance of an unknown piece of equipment

## INTRODUCTION

Within all of the equipment you use, the DMM, the AD2, and even batteries, there are **internal resistances**. The equipment has been designed so that in most cases, your measurements will not be altered by the internal resistances of the equipment. However, there may be cases where the internal resistances of the equipment actually affect your measurements. As a practicing engineer, you must be aware of these internal resistances as a possible cause of error in your measurements. You must also learn how to measure such internal resistances so that you can work around these limitations if necessary.

This lab will introduce you to the internal resistances in the lab equipment you have encountered thus far in lab and teach you ways to measure them. In this course, we use the Digital Multimeter (DMM) to measure voltage, current, and resistance. In each mode (V, A,  $\Omega$ ), there is a different internal resistance within the DMM. For each mode, the internal resistance is negligible and can ordinarily be ignored in our day-to-day measurements. However, there are limits for each mode of the DMM due to these internal resistances, which you must be aware of as you encounter and attempt to measure the various circuits you will build. These limits similarly apply to the AD2.

### **Maximum Power Transfer Theory**

In order to achieve the **maximum load power** in a DC circuit, the load resistance must equal the driving resistance, that is, the internal resistance of the source (Thévenin resistance). Any load resistance value above or below this will produce a smaller load power. **System efficiency** ( $\eta$ ), which can be defined as the ratio of load power to total power, is **50%** at the maximum power case. This is because the load and the internal resistance form a basic series loop, and as they have the same value, they must exhibit equal currents and voltages, and hence equal power dissipation. As the load increases in resistance beyond the maximizing value, the load voltage will rise; however, the load current will drop by a greater amount yielding a lower load power. Although this is not the maximum load power, this will represent a larger percentage of total power produced, and thus a greater efficiency (the ratio of load power to total power).

Any circuit can be thought of as a “black box” of sorts, where you may not know anything about the exact components it is made of or what it does. In many cases, you will be unable to access the internal circuitry of a device such as the DMM or power supply. From previous labs, we know that we can represent any circuit with its Thévenin equivalent circuit. The point at which the load resistance matches the internal resistance of the black box circuit (Thévenin resistance) is when maximum power transfer occurs, as shown below in **Figure 1**. This knowledge will prove to be extremely useful in attempting to determine the internal resistances of the equipment in these labs.

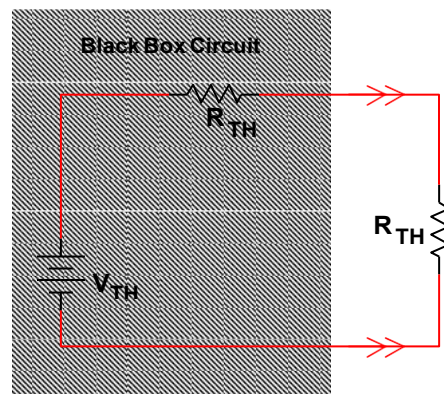


Figure 1 – Maximum Power Transfer

**The DMM in Voltage Mode**

When a DMM is set to measure voltage, a resistance internal to the DMM ( $R_V$ ) is placed in **parallel** with the circuit it is measuring, as shown in **Figure 2**. Ideally, we would like  $R_V$  to be enormous, an open circuit in fact. Instead, it has a very large finite value.  $R_V$  draws a small amount of current from the circuit it measures, and the internal meter calculates the voltage across  $R_V$ , which is of course the voltage across the circuit one is measuring since  $R_V$  is in parallel with the circuit under test. Because  $R_V$  is large, it has little effect on the circuit one is measuring, unless  $R_V$  is close in size to the resistor being measured. The effect  $R_V$  has on the circuit being measuring is called “loading” because an additional load is placed on the circuit one is measuring. In this lab, we will determine  $R_V$  using **Maximum Power Transfer Theory**.

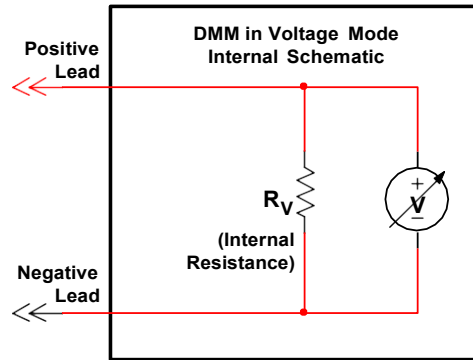


Figure 2 – DMM Reading Voltage

**The DMM in Current Mode**

When a DMM is set to measure current, an internal resistance ( $R_A$ ) is placed in **series** with the circuit it is measuring. This is why we interrupt or break the circuit we are measuring current through. The current must flow into the meter through  $R_A$ . The schematic of the internals of the DMM in current mode is shown in **Figure 3**. Ideally, we would like  $R_A$  to be very small, a short circuit in fact. Instead, it has a small finite value.  $R_A$  allows all of the current from the circuit to flow into the meter and then back into the circuit one is measuring. Because  $R_A$  is very small, a very small amount of voltage is dropped across it, having little effect on the circuit one is measuring, unless  $R_A$  is close in size to the resistor one is measuring the current through. The effect of the internal resistor  $R_A$  has on the circuit one is measuring is called the resistance burden because it is burdening the circuit one is measuring. In this lab, we will measure  $R_A$  using **Maximum Power Transfer Theory**.

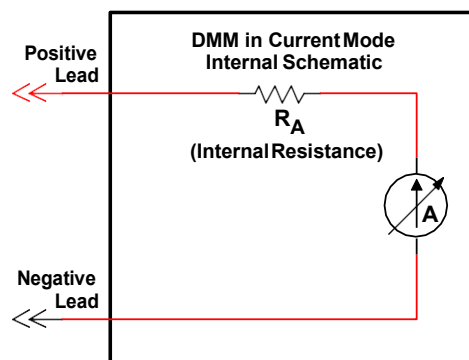


Figure 3 – DMM Reading Current

**Regulated and Unregulated Voltage Sources**

In class, the voltage sources we have studied do not have a current limit. No matter what resistance we attach to our theoretical voltage sources, the proper current is always supplied. However, any practical voltage source (battery, power supply, or generator) has internal resistances. These resistances limit the battery from producing infinite current. **Figure 4** shows the Thévenin equivalent circuit for any practical voltage source. While internally the voltage source may have a complicated configuration of current sources and resistances, they are all summed up in the Thévenin equivalent voltage source  $V_{TH}$  and resistance  $R_{TH}$ . The internal resistance of any power supply  $R_{TH}$  is designed to be as small as possible, from a few ohms to fractions of an ohm, so that little voltage drop occurs and the proper voltage is supplied to the circuit. In this lab, we will measure  $V_{TH}$  and  $R_{TH}$  of both the AD2 and a battery.

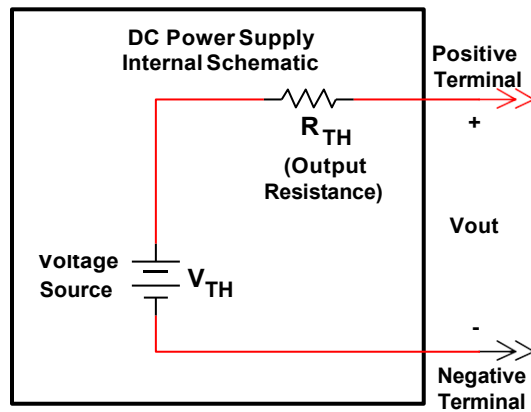


Figure 4 – DC Power Supply Thévenin Equivalent Circuit

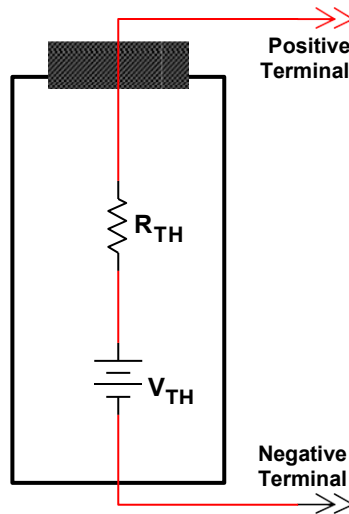


Figure 5 – Battery Thévenin Equivalent Circuit

**PRELAB**

**Part I – Maximum Signal Transfer**

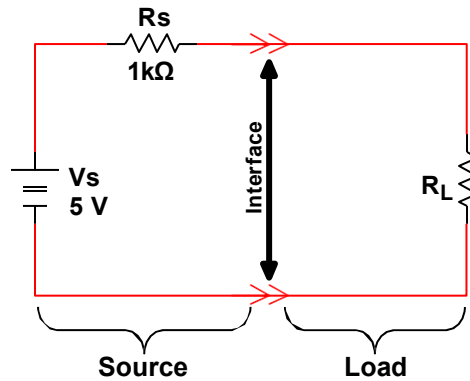


Figure P.1.1 – Problem #1

For the circuit in **Figure P.1.1**,  $V_S$  and  $R_S$  are fixed at the values shown in the schematic.

1. For each value of  $R_L$  listed in the table, **hand calculate**  $V_{R_S}$ ,  $V_{R_L}$ ,  $I_{R_L}$ , and the power dissipated (or generated) by the voltage source,  $R_S$ , and  $R_L$ .
2. **Calculate** the system efficiency  $\eta$  using the data calculated in step 1.

$R_S$	$R_L$	$V_{R_S}$	$V_{R_L}$	$I_{R_L}$	$P_{V_S}$	$P_{R_S}$	$P_{R_L}$	$\eta$
1k $\Omega$	0 $\Omega$							
1k $\Omega$	250 $\Omega$							
1k $\Omega$	500 $\Omega$							
1k $\Omega$	1k $\Omega$							
1k $\Omega$	1.25k $\Omega$							
1k $\Omega$	1.5k $\Omega$							
1k $\Omega$	2k $\Omega$							
1k $\Omega$	1M $\Omega$							

Table P.1.1 – Prelab Data Table 1

**Answer** the following questions regarding the table calculations:

1. What value of  $R_L$  caused the highest amount of **current** in the circuit?
2. What value of  $R_L$  caused the highest amount of **voltage** across the interface?
3. What value of  $R_L$  caused the greatest amount of **power** to be transferred from the source to  $R_L$ ?
  - a. When this occurred, was  $R_L < R_S$ ,  $R_L = R_S$ , or  $R_L > R_S$ ?
  - b. When this occurred, what do you notice about the voltage drop across  $R_S$  and  $R_L$ ?
  - c. When this occurred, what do you notice about the current through the circuit, as compared to the maximum current in the circuit?
  - d. When this occurred, what is the system efficiency?
4. Assume you have a circuit identical to that of **Figure P.1.1**. Assume now that you could not directly measure the voltage across  $R_S$ , and you do not know its value. Assume  $R_L$  was a potentiometer and you set up a DMM to measure the voltage across it. Could you determine the value of  $R_S$ ? If so, **explain** how you would do this.

## Part II – Determining $V_{TH}$ and $R_{TH}$ Numerically

In **Part I** of this prelab, we were given the value of  $R_S$  (the resistance of the source) and the value of  $V_S$  (internal voltage of the source). However, we normally do not know the value of  $R_S$  or  $V_S$ , because these characteristics are contained within our power source. We only have the two terminals sticking out of the power source (positive and negative), so measuring  $R_S$  directly is not possible. We will now explore a method for finding  $R_S$ , which involves measuring the voltage and current coming out of our battery or power supply itself.

Consider the circuit setup in **Figure P.2.1** below. We do not know what  $V_{TH}$  or  $R_{TH}$  are inside the voltage source. However, we can attach different size resistors to the voltage source and measure  $I_L$  and  $V_L$  (the usefulness of these measurements will be explained shortly). For five possible values of  $R_L$ , we have measured values for  $I_L$  and  $V_L$  as shown in **Table P.2.1**.

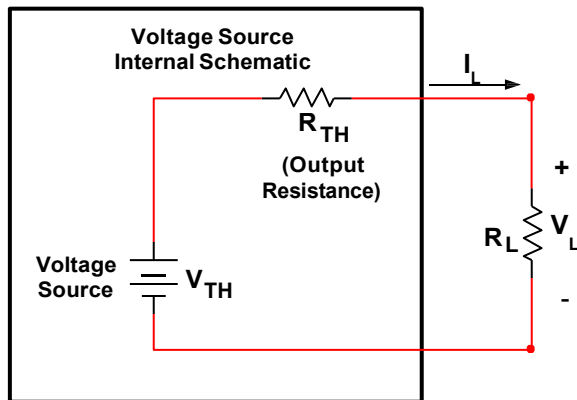


Figure P.2.1 – Circuit to Measure  $R_{TH}$

$R_L$	$I_L$	$V_L$
10M $\Omega$	0.0mA	5.000V
1k $\Omega$	4.9mA	4.990V
500 $\Omega$	9.9mA	4.985V
250 $\Omega$	19.8mA	4.955V
100 $\Omega$	49.0mA	4.920V

Table P.2.1 – Values of  $I_L$  and  $V_L$  for Various  $R_L$

We need a way to relate the data we have collected back to the circuit we have in **Figure P.2.1**. We can easily use KVL to relate the values of  $R_{TH}$  and  $V_{TH}$  (our unknown variables) to  $R_L$  and  $V_L$  (our measured, known variables).

1. For this prelab problem, use **KVL** on the circuit in **Figure P.2.1** to generate an equation for the voltages in the loop in terms of the variables  $V_{TH}$ ,  $R_{TH}$ ,  $R_L$ , and  $V_L$ . For example, using Ohm's law, we know the voltage across the internal source resistor,  $V_{R_{TH}} = R_{TH} \times I_L$ , so we can eliminate  $V_{R_{TH}}$  from our KVL equation.
2. The next step is to **solve the KVL equation** you have generated for  $V_L$ . You should have an equation that is of the form of a line ( $y=mx+b$ , where  $y = V_L$ ,  $m = R_{TH}$ , etc).
3. Now, **use regression analysis** to find the approximate values of  $R_{TH}$  and  $V_{TH}$ . To do this, refer to the tutorial: "**Using MS Excel to solve a system of equations with linear regression**" that is on the lab website.

What to turn in for this problem:

1. Your KVL equation for the circuit in **Figure P.2.1** and all work getting it to be in  $y=mx+b$  form.
2. A plot of the regression analysis you did in **Excel** showing the trendline, equation, and  $R^2$ .
3. Using what you did in Excel, what is the value for  $R_{TH}$  in the circuit in **Figure P.2.1**?
4. From the data and circuit, we can see that we expect this to be a 5V battery. However, what load resistance  $R_L$  could we attach to this and get only 2.5V across it? Essentially, for what values of  $R_L$  would this battery **cease to look like a 5V battery**?

**LAB**

**Part I – Determining the Internal Resistance of the DMM in Voltage Mode**

In the prelab, we learned the DMM, when in voltage mode, appears to have a large internal resistance  $R_V$  in **parallel** with any circuit we are measuring. We wish to determine  $R_V$  by using what we learned about maximum power transfer from the prelab.

**Note:** You will be using multiple potentiometers throughout this lab. Their resistance values are extremely sensitive to touch, and proper care must be taken to obtain accurate measurements. It is usually easiest to measure the resistance of a potentiometer by disconnecting all wires attached to it, and measuring its resistance while it is actually still in the breadboard.

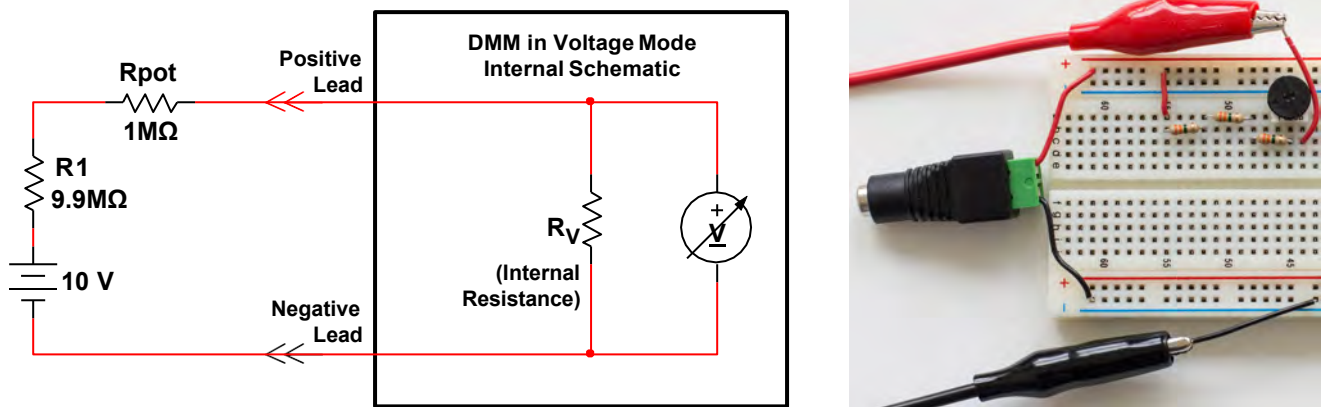


Figure 1.1 – Experimental Setup

1. **Set up** the circuit in **Figure 1.1**. For  $R_1$ , use three  $3.3M\Omega$  resistors in series.
2. Plug in the DC Power Supply and set it to 10 V
3. **Attach** the negative terminal of the DMM to the negative terminal of the power supply and the positive terminal of the DMM to the potentiometer as shown above.
4. **Set** the DMM to voltage mode with auto-range enabled.
5. Initially, set  $R_{POT}$  to its **lowest value** and **record** the reading from the DMM as Initial  $V_{RPOT}$ .
6. Using what you have learned in the prelab, what value will the DMM read if you adjust  $R_{POT}$  so that  $R_{POT} + 9.9M\Omega = R_V$ ? **Determine** this value and fill it into **Table 1.1**.
7. **Adjust**  $R_{POT}$  until you determine  $R_V$ , **record** the voltage reading as Final  $V_{RPOT}$ , and **measure** the value of  $R_{POT}$ .

**Note:** Remember you must disconnect  $R_{POT}$  from the circuit in order to measure it using the DMM in  $\Omega$

mode.

<i>Initial <math>V_{RPOT}</math></i>	<i>V at <math>R_L = R_V</math></i>	<i>Final <math>V_{RPOT}</math></i>	<i><math>R_{POT}</math></i>

Table 1.1 – DMM in Voltage Mode Data



**Part II – Determining the Internal Resistance of the DMM in Current Mode**

In the prelab, we learned the DMM, when in current mode, appears to have a small internal resistance  $R_A$  in **series** with any circuit we are measuring. We wish to determine  $R_A$  by using what we learned about maximum power transfer from the prelab.

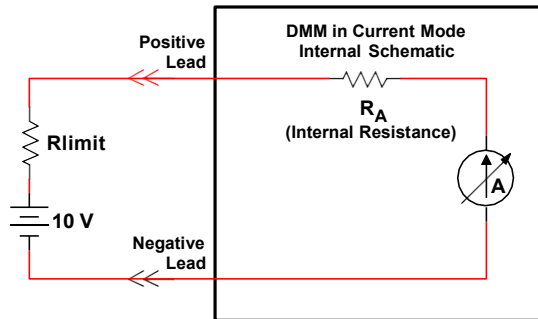


Figure 2.1 – Experimental Setup without Load


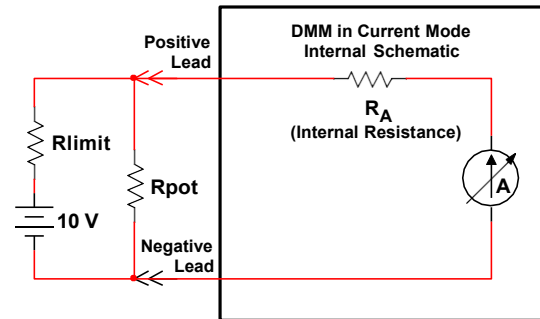
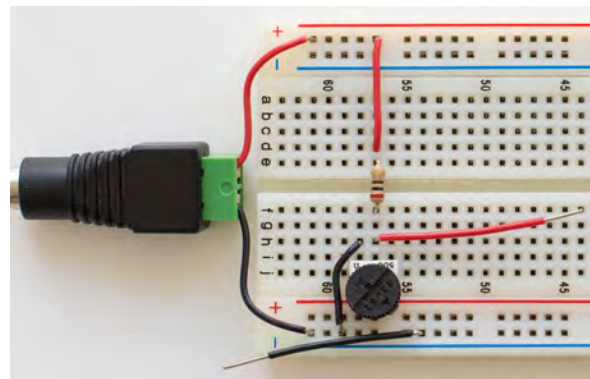


Figure 2.2 – Experimental Setup with Load

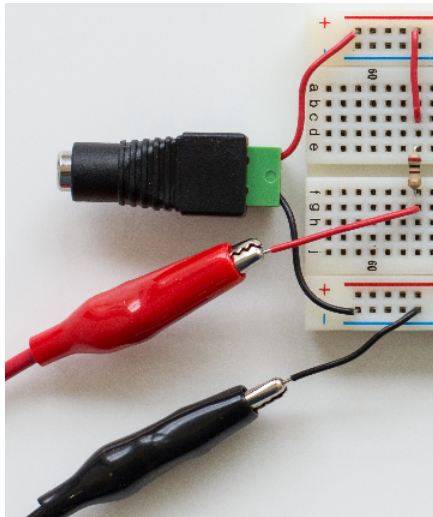

1. **Set up** the circuit in **Figure 2.1**, attaching the DMM to measure the current through  $R_{LIMIT}$ .
2. **Calculate** a value for resistor  $R_{LIMIT}$  in **Figure 2.1** using Ohm's law. The goal is to let **only** 50mA flow into the DMM. **Assume**  $R_A$  is  $0\Omega$  for this calculation.  
*Note: Because  $R_A$  is actually very small, a very large amount of current would flow into the DMM if a 10V source was applied to it directly.  $R_{LIMIT}$  limits the amount of current into the DMM to 50mA, which will protect the DMM from blowing a fuse.*
3. **Record** the exact value of the current through  $R_{LIMIT}$  as  $I_{MAX}$ . Remember that the DMM does **not** have an auto-range button for measuring current.
4. **Attach** the smallest range potentiometer  $R_{POT}$  available in your kit as the circuit's load as shown in **Figure 2.2**. Set it to its highest value at first.  
*Note: Make certain to turn off the power supply when you make changes to the circuit.*
5. **Adjust** the value of  $R_{POT}$  until the DMM reads  $\frac{1}{2}$  of the  $I_{MAX}$  you found in Step 3.
6. **Turn off** the circuit, then disconnect and measure the **resistance** of  $R_{POT}$ .
7. This value of  $R_{POT}$  is **equal** to the value of  $R_A$ . **Why** is this true?


$R_{LIMIT}$	$I_{MAX}$	$R_{POT}$

Table 2.1 – DMM in Current Mode Data



**Part III – Determining the Internal Resistance of an Unregulated Voltage Source (Battery)**

In the prelab, we learned that any voltage source has some small internal resistance that limits its output current. We wish to determine the internal Thévenin voltage ( $V_{TH}$ ) and resistance ( $R_{TH}$ ) of a standard 1.5V AA Battery by using what we learned about maximum power transfer from the prelab.

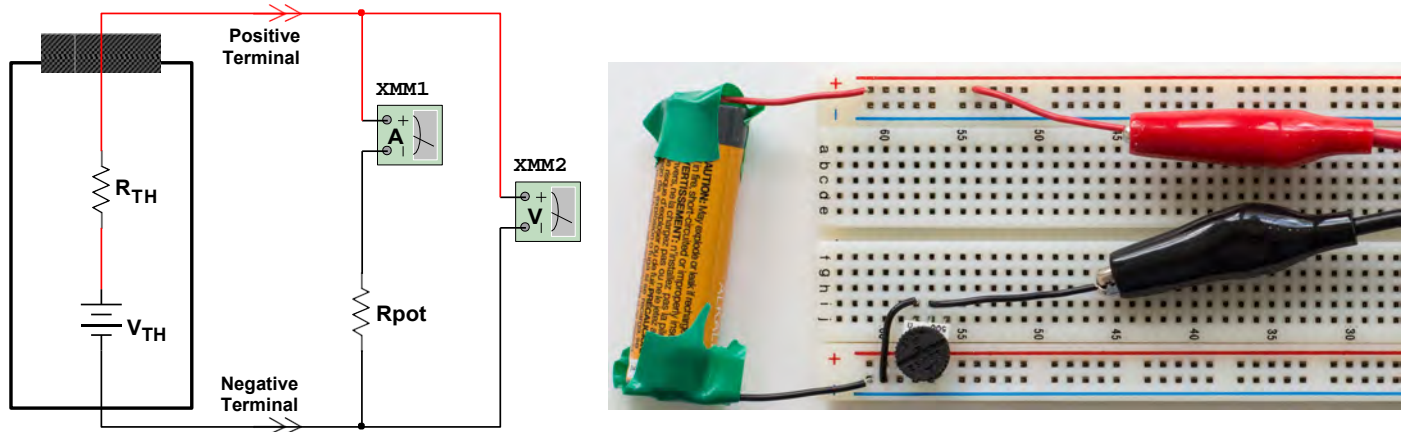

**Figure 3.1 – Experimental Setup**

1. **Set up** the circuit in **Figure 3.1**.
  - a. Your DMM (in **current** mode, A) is represented by the multimeter **XMM1** in the schematic.
  - b. Use the WaveForms "voltmeter" tab as a second DMM measuring voltage. This is represented by **XMM2** in the schematic.
  - c. **Use** the **AA battery** supplied in your toolkit, note its rated voltage is 1.5V.
  - d. **Use** tape to secure wires to the AA battery. It's recommended that you stick the wire to the tape first, and then tape it to the battery second.
    - i. Check your wire connections are secure by using your DMM, measuring voltage. You should get around 1.5V.
  - e. **Initially**, use a **10MΩ** resistor for R POT.
2. **Ensure** that the current meter reads **0A** with the 10MΩ resistor for R POT.  
**Note:** The value that the voltage meter now reads is the Thévenin equivalent voltage ( $V_{TH}$ ). R\_POT is so large that no current may flow through it or R\_TH. The battery basically sees an open circuit.
3. **Record** the value from the DMM measuring voltage as  $V_{TH}$ .
4. **Replace** the 10MΩ resistor with a **500Ω** potentiometer for better precision in the next step.
5. **Lower** the value of the potentiometer until current begins to flow into R\_POT (a fewmA).
  - a. **Record** the current reading from the DMM in **Table 3.1**.
  - b. **Record** the voltage across R\_POT in **Table 3.1**.
  - c. **Disconnect** R\_POT and measure its resistance.
6. **Repeat** Step 5, lowering the potentiometer resistance until you draw about 50mA.  
**Warning:** Very low values of R\_POT will cause a large amount of current to be drawn from the battery. Do not lower R\_POT to values that draw more than 50mA as this will essentially short the terminals of the battery together, causing it to heat up, and risk potential injury to you!
7. **Record** the voltage across and the current through R\_POT for each of these four values. Then, adjust the potentiometer to **four** points between the point where you draw 50mA and a few mA.
8. During your Post-Lab Analysis, **determine** R\_TH using the **numerical method in Excel** outlined in **Part II** of the prelab.

$R_{POT}$	$I_{RPOT}$	$V_{RPOT}$

**Table 3.1 – Unregulated AA Battery Data**

**Part IV – Determining the Internal Resistance of a Regulated Voltage Source (DC Power Supply)**

The KLY DC power supply is considered a **regulated** voltage source, as compared to a battery, because it has additional circuitry within it to maintain the desired voltage set by the user no matter the load applied across it. This makes it so that we must stress the power supply using very small resistances to determine the very small  $R_{THEV}$  internal resistance of this source.

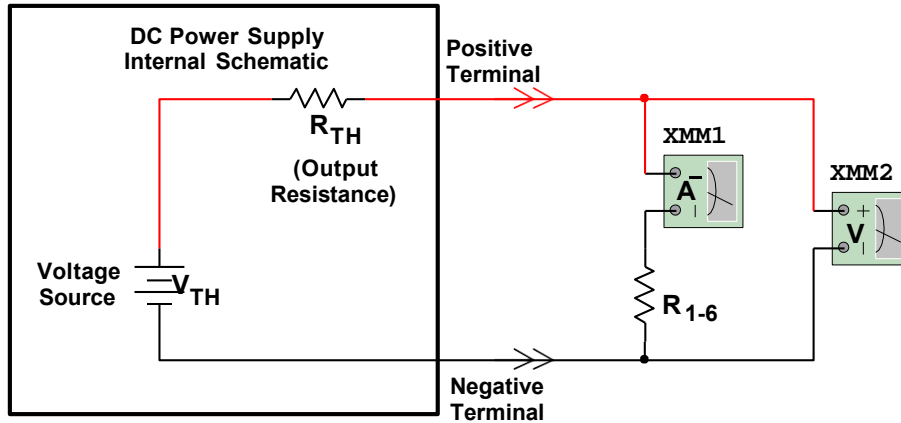


Figure 4.1 – Experimental Setup

1. **Set up** the circuit in **Figure 4.1**.
  - a. The DMM (in **current** mode, A) is represented by the multimeter **XMM1** in the schematic.
  - b. A **second** DMM (in **voltage** mode, V) is represented by **XMM2** in the schematic. This will be the AD2.
  - c. **Use** the KLY 2402000 power supply as the source. For each measurement you will set the voltage as low as it will go before turning it off. This should be around **3.5V**. Turn the voltage 'off' before attaching the next components.
2. **Start** by using the **9.1MΩ** resistor. Apply the 3.5V to the resistor, and record the voltage and current across it. Make sure to turn off the power supply once you have recorded these measurements.
3. The value that the voltage meter now reads is the Thévenin equivalent voltage ( $V_{TH}$ ). This is because  $R_L$  is so large that very little current may flow through it or  $R_{TH}$ . The power supply essentially sees an open circuit. **Record**  $V_{TH}$ .
4. **Replace**  $R_L$  with five different resistances:  $R_2 - R_6$ . Record the current and voltage through each resistor. Again, remember to turn off the Power Supply as you change each resistor.
5. During your Post-Lab Analysis, **determine**  $R_{TH}$  using the **numerical method in Excel** outlined in **Part II** of the prelab. The value for  $R_{TH}$  will be extremely small.

$R_L$	$I_L$	$V_L$
9.1MΩ		
270kΩ		
10kΩ		
3.3kΩ		
1kΩ		
680Ω		

Table 4.1 – Regulated Power Supply Data

**POST-LAB ANALYSIS**

1. **Complete** the following **table** of the internal resistances for each piece of lab equipment you have worked with in this lab and include it in your report. Keep it for future reference.

<i>Lab Equipment</i>	<i>Internal Resistance</i>
<i>Handheld DMM in Voltage Mode</i>	
<i>Handheld DMM in Current Mode</i>	
<i>1.5V AA Battery</i>	
<i>KLY 2402000 DC Power Supply</i>	

Table A.1 – Internal Resistances

2. Look up the datasheet for your DMM to find the specified values for the internal resistances in voltage mode. This is typically referred to as “Input Resistance” because it is the resistance of the equipment looking “inward” towards the two terminals of the device.
3. For each piece of equipment, discuss the situations where the internal resistance will disrupt or give you inexact values for your measurements of circuits you may build in the lab. Give examples with numerical results to prove your point.
4. For **Part III** and **Part IV** of the lab, what is your margin of error (based on precision of the equipment, and  $R^2$  from excel). **Explain** how you arrived at your calculation of error margin.