

---

# THE GEORGE WASHINGTON UNIVERSITY

---

WASHINGTON, DC

SCHOOL OF ENGINEERING AND APPLIED SCIENCE  
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING  
ECE 2110: CIRCUIT THEORY LABORATORY

Experiment #5:  
*Thévenin's Theorem, Mesh Current, and Node Voltage Analysis*

## EQUIPMENT

<i>Lab Equipment</i>	<i>Equipment Description</i>
(1) DC Power Supply	Keysight E36311A Triple Output DC Power Supply
(1) Digital Multimeter (DMM)	Agilent 34460A (DMM)
(1) Breadboard	Prototype Breadboard
(3) Test Leads	Banana to Alligator Lead Set

Table 1 – Equipment List

## COMPONENTS

<i>Type</i>	<i>Value</i>	<i>Symbol Name</i>	<i>Multisim Part</i>	<i>Description</i>
Resistor	750 $\Omega$	R <sub>1</sub>	Basic/Resistor	---
Resistor	1k $\Omega$	R <sub>2</sub>	Basic/Resistor	---
Resistor	1.5k $\Omega$	R <sub>3</sub>	Basic/Resistor	---
Resistor	3k $\Omega$	R <sub>4</sub>	Basic/Resistor	---
Resistor	4k $\Omega$	R <sub>5</sub>	Basic/Resistor	---
Resistor	10k $\Omega$	R <sub>6</sub>	Basic/Resistor	---
Resistor	12k $\Omega$	R <sub>7</sub>	Basic/Resistor	---
Resistor	15k $\Omega$	R <sub>8</sub>	Basic/Resistor	---

Table 2 – Component List

## OBJECTIVES

- To understand Thévenin's theorem of equivalent circuits
- To analyze and reduce three DC circuits to their Thévenin equivalent circuits by hand
- To analyze and reduce three DC circuits to their Thévenin equivalent circuits with Multisim
- To analyze and reduce three DC circuits to their Thévenin equivalent circuits in la

## INTRODUCTION

In this lab, you must find the Thévenin and Norton equivalents for three separate circuits. You will first perform the analysis by hand using the techniques that you have learned in lecture and in your homework. Then, you will simulate the circuits in Multisim, using it to find the Thévenin and Norton equivalents. Finally, you will build the three circuits in lab and measure them to find the Thévenin and Norton equivalents. In your lab report, you will compare and analyze the results from each technique.

### Thévenin's Theorem

**Thévenin's Theorem** for DC circuits states that any two port linear network may be replaced by a single voltage source with an appropriate internal resistance. The Thévenin equivalent will produce the same load current and voltage as the original circuit to any load. Consequently, if many different loads or subcircuits are under consideration, using a Thévenin equivalent usually proves to be a much quicker method of analysis. Any complex circuit consisting of multiple sources and components can be reduced to a single voltage source, the Thévenin voltage, in series with its internal resistance, the Thévenin resistance.

The **Thévenin voltage**,  $V_{TH}$ , is found by determining the open-circuit output voltage. The **Thévenin resistance**,  $R_{TH}$ , is found by replacing any DC sources with their internal resistances and determining the resulting combined resistance as seen from the two ports using standard series-parallel analysis techniques. A voltage source would be replaced by a short, zero resistance, and a current source would be replaced by an open, infinite resistance. In the laboratory, the Thévenin resistance may be found using an ohmmeter (again, replacing the sources with their internal resistances) or by using the matched load technique. The matched load technique involves replacing the load with a variable resistance and then adjusting it until the load voltage is precisely one-half of the unloaded voltage. This would imply that the other half of the voltage must be dropped across the equivalent Thevenin resistance, and as the Thevenin circuit is a simple series loop then the two resistances must be equal as they have identical currents and voltages.

### Norton's Theorem

**Norton's Theorem** for DC circuits states that any two port linear network may be replaced by a single current source with an appropriate internal resistance in parallel. It is closely related to Thévenin's Theorem, and either simplified representation works equally well. Any complex circuit consisting of multiple sources and components can be reduced to a single current source, the Norton or short-circuit current, in parallel with its internal resistance, which is the same as the Thévenin resistance.

The **Norton current** is found by determining the short-circuit output current,  $I_{sc}$ . The internal resistance can be determined in the same manner as was explained above for the Thévenin resistance.

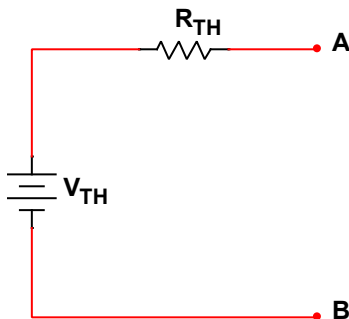


Figure 1 – Thévenin Equivalent Circuit

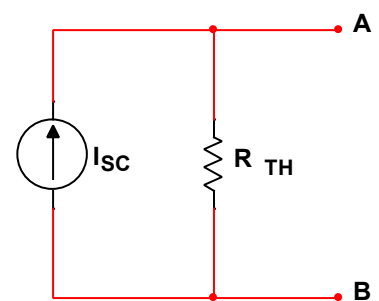


Figure 2 – Norton Equivalent Circuit

### Mesh Current Analysis

Multi-source DC circuits may be analyzed using a mesh current technique. The process involves identifying a minimum number of small loops such that every component exists in at least one loop. **Kirchhoff's Voltage Law** is then applied to each loop, meaning that the algebraic sum of the voltages around each loop must equal zero. The loop currents are referred to as mesh currents as each current interlocks or meshes with the surrounding loop currents. As a result, there will be a set of simultaneous equations created, an unknown mesh current for each loop. Once the mesh currents are determined, various branch currents and component voltages may be derived.

### Node Voltage Analysis

Multi-source DC circuits may be analyzed using a node voltage technique. The process involves identifying all of the circuit nodes, a node being a point where various branch currents combine. A reference node, usually ground, is included. **Kirchhoff's Current Law** is then applied to each node, meaning that the algebraic sum of the currents into and out of each node must equal zero. Consequently, a set of simultaneous equations are created with an unknown voltage for each node with the exception of the reference. In other words, a circuit with a total of five nodes including the reference will yield four unknown node voltages and four equations. Once the node voltages are determined, various branch currents and component voltages may be derived.

### How to Use All Three DC Voltage Outputs

For Part II of this lab, you will need to build a circuit that has three separate voltage sources. It is very important that you know how to properly use all three of the voltage outputs from the DC power supply simultaneously before attempting to do so in lab.

Remember that the KEYSIGHT E36311A Triple Output DC Power Supply has **6V**, **25V**, and **-25V** outputs. Because the positive and negative sources are independent, a common ground is necessary to ensure that there are no "floating" reference points in the circuit. If the negative sides of the voltage sources are grounded in your schematic, they need to be tied together to the same ground in lab. To do this, simply wire the common (black) terminal from each side together to the green **earth ground** terminal in the middle as shown below in **Figure 3**.



Figure 3 – DC Power Supply Connections

**PRELAB**

This prelab consists of three circuits to be reduced using Thévenin's Theorem. You are required to complete both hand calculations and Multisim simulations before coming to lab. **This prelab requires more analysis than previous labs; please allocate the proper amount of time to complete it early on.**

**Part I – Circuit #1 Analysis**

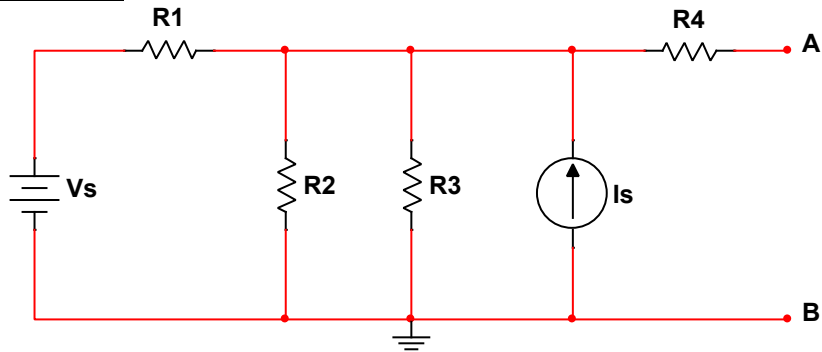


Figure P.1.1 – Circuit #1

In **Figure P.1.1**, the voltage source  $V_s = 6V$  and the current source  $I_s = 10\text{ mA}$ .

1. **Calculate** the following from the perspective of terminals A and B. **Show all work.**
  - a. Thévenin voltage ( $V_{TH}$ )
  - b. Thévenin resistance ( $R_{TH}$ )
  - c. Norton current, also called the short-circuit current ( $I_{SC}$ )
2. **Use** your results to fill in the appropriate values for **Figure P.1.2** and **Figure P.1.3** below:

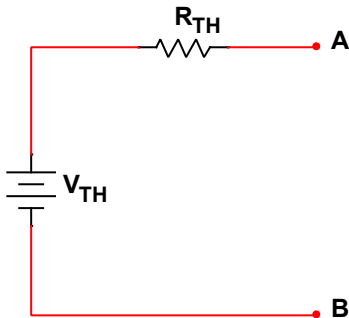


Figure P.1.2 – Thévenin Equivalent of Circuit #1

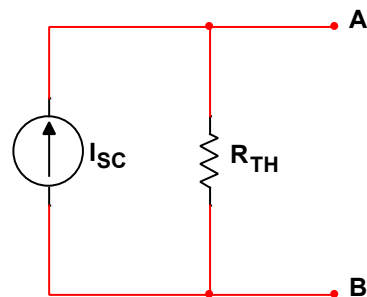


Figure P.1.3 – Norton Equivalent of Circuit #1

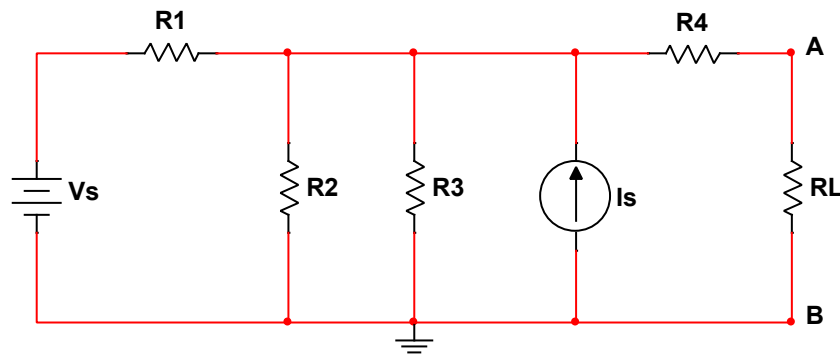


Figure P.1.4 – Circuit #1 with Load Resistor Attached

3. Calculate the **voltage across** and **current through**  $R_L$  for the circuit in **Figure P.1.4**, which has a  $1k\Omega$  load resistor  $R_L$  attached across terminals A and B.

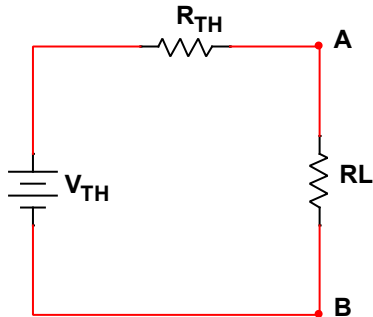


Figure P.1.5 – Thévenin Equivalent with Load Resistor

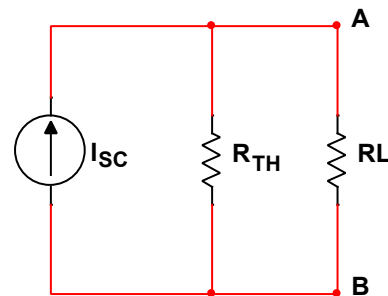


Figure P.1.6 – Norton Equivalent with Load Resistor

4. Calculate the **voltage across** and **current through**  $R_L$  for these circuits, which have a  $1k\Omega$  load resistor  $R_L$  attached across terminals A and B.
5. **Simulate** the circuit from **Figure P.1.1** in Multisim:
- Use the tutorial on the lab website (**Multisim Tutorial #2: Using Multisim to find  $V_{TH}$ ,  $I_{SC}$ ,  $R_{TH}$** ) to learn how to find  $V_{TH}$ ,  $I_{SC}$ , and  $R_{TH}$  for a circuit in Multisim.
  - Build** the circuit in **Figure P.1.1** in Multisim and find its  $V_{TH}$ ,  $I_{SC}$ , and  $R_{TH}$ .
  - Build** the equivalent circuits in **Figure P.1.2** and **Figure P.1.3** in Multisim.
  - In Multisim, attach a  $1k\Omega$  load resistor ( $R_L$ ) to the circuit as you did in **Figure P.1.4**. **Measure** and **record** the simulated voltage across and current through  $R_L$ .
  - In Multisim, attach  $1k\Omega$  load resistors ( $R_L$ ) to the equivalent circuits in **Figure P.1.5** and **Figure P.1.6**. **Measure** and **record** the simulated voltage across and current through  $R_L$ .

Electrical Quantity	$V_{TH}$	$R_{TH}$	$I_{SC}$	Original Circuit		Equivalent Circuit	
				$V_{RL}$	$I_{RL}$	$V_{RL}$	$I_{RL}$
Calculated							
Simulated							
Percent Error							

Table P.1 – Circuit #1 Data

**Part II – Circuit #2 Analysis**

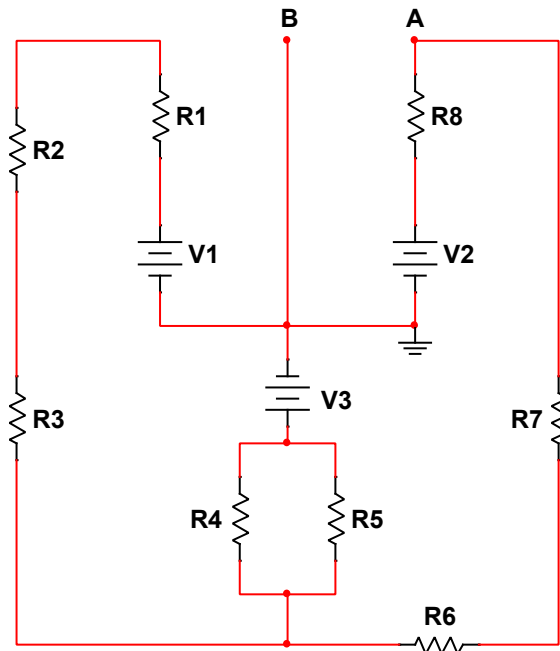


Figure P.2.1 – Circuit #2

In **Figure P.2.1**, the voltage sources  $V_1 = 3V$ ,  $V_2 = 6V$ , and  $V_3 = -6V$ .

1. **Calculate** the following from the perspective of terminals A and B. **Show all work.**
  - a. Thévenin voltage ( $V_{TH}$ )
  - b. Thévenin resistance ( $R_{TH}$ )
  - c. Norton current, also called the short-circuit current ( $I_{sc}$ )
2. **Use** your results to fill in the appropriate values and draw the **Thévenin** and **Norton equivalents** as you did in Part I.
3. **Attach** a  $1k\Omega$  load resistor  $R_L$  across terminals A and B in **Figure P.2.1** and **calculate** the **voltage across** and **current through**  $R_L$  for the new circuit.
4. **Attach** a  $1k\Omega$  load resistor  $R_L$  across terminals A and B in the equivalent circuits that you drew and **calculate** the **voltage across** and **current through**  $R_L$  for the new circuits.
6. **Simulate** the circuit from **Figure P.2.1** in Multisim:
  - a. **Build** the circuit in **Figure P.2.1** in Multisim and find its  $V_{TH}$ ,  $I_{sc}$ , and  $R_{TH}$ .
  - b. **Build** the equivalent circuits in Multisim.
  - c. In Multisim, attach a  $1k\Omega$  load resistor ( $R_L$ ) to the original circuit. **Measure** and **record** the simulated voltage across and current through  $R_L$ .
  - d. In Multisim, attach  $1k\Omega$  load resistors ( $R_L$ ) to the equivalent circuits. **Measure** and **record** the simulated voltage across and current through  $R_L$ .

Electrical Quantity	$V_{TH}$	$R_{TH}$	$I_{sc}$	Original Circuit		Equivalent Circuit	
				$V_{RL}$	$I_{RL}$	$V_{RL}$	$I_{RL}$
<b>Calculated</b>							
<b>Simulated</b>							
<b>Percent Error</b>							

Table P.2 – Circuit #2 Data

**Part III – Circuit #3 Analysis**

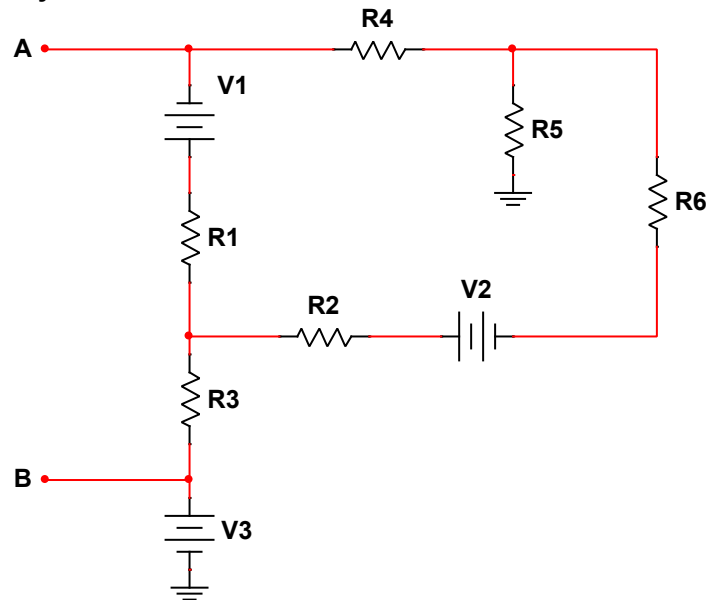


Figure P.3.1 – Circuit #3

In **Figure P.3.1**, the voltage sources **V1 = 3V**, **V2 = 6V**, and **V3 = 9V**.

1. **Calculate** the following from the perspective of terminals A and B. **Show all work.**
  - a. Thévenin voltage ( $V_{TH}$ )
  - b. Thévenin resistance ( $R_{TH}$ )
  - c. Norton current, also called the short-circuit current ( $I_{SC}$ )
2. **Use** your results to fill in the appropriate values and draw the **Thévenin** and **Norton equivalents** as you did in Part I and Part II.
3. **Attach** a 1k $\Omega$  load resistor  $R_L$  across terminals A and B in **Figure P.3.1** and **calculate** the **voltage across** and **current through  $R_L$**  for the new circuit.
4. **Attach** a 1k $\Omega$  load resistor  $R_L$  across terminals A and B in the equivalent circuits that you drew and **calculate** the **voltage across** and **current through  $R_L$**  for the new circuits.
7. **Simulate** the circuit from **Figure P.3.1** in Multisim:
  - a. **Build** the circuit in **Figure P.3.1** in Multisim and find its  $V_{TH}$ ,  $I_{SC}$ , and  $R_{TH}$ .
  - b. **Build** the equivalent circuits in Multisim.
  - c. In Multisim, attach a 1k $\Omega$  load resistor ( $R_L$ ) to the original circuit. **Measure** and **record** the simulated voltage across and current through  $R_L$ .
  - d. In Multisim, attach 1k $\Omega$  load resistors ( $R_L$ ) to the equivalent circuits. **Measure** and **record** the simulated voltage across and current through  $R_L$ .

Electrical Quantity	$V_{TH}$	$R_{TH}$	$I_{SC}$	Original Circuit		Equivalent Circuit	
				$V_{RL}$	$I_{RL}$	$V_{RL}$	$I_{RL}$
<b>Calculated</b>							
<b>Simulated</b>							
<b>Percent Error</b>							

Table P.3 – Circuit #3 Data

**LAB**

**Part I – Circuit #1 Measurements**

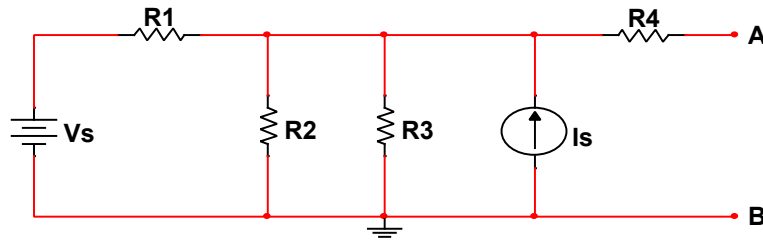


Figure 1.1 – Circuit #1

1. **Build** the circuit from **Part I** of the prelab shown again in **Figure 1.1** on a breadboard.
2. **Measure** the circuit to find  $V_{TH}$ ,  $R_{TH}$ , and  $I_{SC}$ .
  - a.  **$V_{TH}$  Measurement:** Use the **DMM** to measure the **voltage** between terminals A and B.
  - b.  **$I_{SC}$  Measurement:** **Switch** the DMM to current mode and **measure** the **current** between terminals A and B.  
**Note:** Remember that the DMM in current mode has a very small internal resistance, such that connecting it directly between terminals A and B short-circuits A to B. This easily gives us the short-circuit current in this case.
  - c.  **$R_{TH}$  Measurement:**
    - i. **Turn off** and **remove** the DC power supply connections used for  $V_s$  and  $I_s$ . ii. **Use** a wire to connect where the voltage source  $V_s$  originally was in your circuit. **Note:** As discussed in the **Introduction**, we must “short” the voltage sources. In real life, however, we cannot simply short the power supply as it would overload it. **\*\*\*You absolutely must remove the power supply before shorting it.\*\*\***
    - iii. **Open** the location where  $I_s$  originally was in your circuit. iv. **Measure** the **resistance** between terminals A and B using the DMM.
3. **Remove** the wire used to short the voltage source and **reconnect** the power supply to the circuit.
4. **Connect** a 1k $\Omega$  load resistor  $R_L$  between terminals A and B and **measure** the **voltage across** and the **current through**  $R_L$ .
5. **Build** the **Thévenin Equivalent** circuit from **Figure P.1.5** with the load  $R_L$  attached.
  - a. **Set** the power supply to  $V_{TH}$ .
  - b. **Measure** the **voltage across** and the **current through**  $R_L$ .
6. **Connect** a resistor between terminals A and B that is **equal** to the **Thévenin resistance** ( $R_{TH}$ ) you calculated. **Measure** the **voltage across** ( $V_{R_{TH}}$ ) and the **current through** ( $I_{R_{TH}}$ ) the resistor.
7. **Record** all measured data in the **Table 1.1** and **calculate** the **percent error** between your simulated and measured results.

Electrical Quantity	$V_{TH}$	$R_{TH}$	$I_{SC}$	$V_{R_{TH}}$	$I_{R_{TH}}$	Original		Equivalent	
						$V_{R_L}$	$I_{R_L}$	$V_{R_L}$	$I_{R_L}$
<b>Calculated</b>									
<b>Simulated</b>									
<b>Measured</b>									
<b>Percent Error</b>									

Table 1.1 – Circuit #1 Data



**Part II – Circuit #2 Measurements**

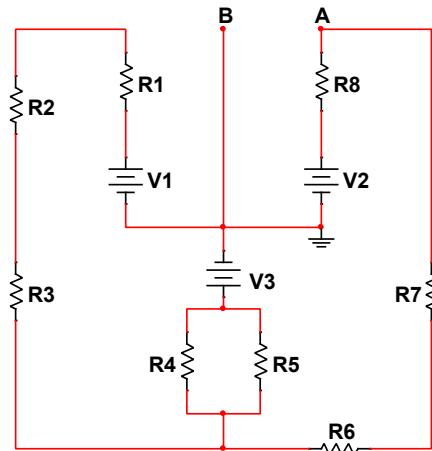


Figure 2.1 – Circuit #2

1. **Build** the circuit from **Part II** of the prelab shown again in **Figure 2.1** on a breadboard.
  - a. Refer to the **Introduction** to recall how to set up your circuit and DC power supply with three voltage sources.
2. **Measure** the circuit to find  $V_{TH}$ ,  $R_{TH}$ , and  $I_{sc}$ .
  - a.  **$V_{TH}$  Measurement:** Use the **DMM** to measure the **voltage** between terminals A and B.
  - b.  **$I_{sc}$  Measurement:** **Switch** the DMM to current mode and **measure** the **current** between terminals A and B.
  - c.  **$R_{TH}$  Measurement:**
    - i. **Turn off** and **remove** the DC power supply connections used for  $V_s$  and  $I_s$ .
    - ii. **Use** a wire to connect where the voltage source  $V_s$  originally was in your circuit.
    - iii. **Open** the location where  $I_s$  originally was in your circuit.
    - iv. **Measure the resistance** between terminals A and B using the DMM.
3. **Remove** the wire used to short the voltage source and **reconnect** the power supply to the circuit.
4. **Connect** a  $1k\Omega$  load resistor  $R_L$  between terminals A and B and **measure** the **voltage across** and the **current through**  $R_L$ .
5. **Build** the **Thévenin Equivalent** as you did for Circuit #1.
  - a. **Set** the power supply to  $V_{TH}$ .
  - b. **Measure** the **voltage across** and the **current through**  $R_L$ .
6. **Connect** a resistor between terminals A and B that is **equal** to the **Thévenin resistance** ( $R_{TH}$ ) you calculated. **Measure** the **voltage across** ( $V_{R_{TH}}$ ) and the **current through** ( $I_{R_{TH}}$ ) the resistor.
7. **Record** all measured data in the **Table 2.1** and **calculate** the **percent error** between your simulated and measured results.

Electrical Quantity	$V_{TH}$	$R_{TH}$	$I_{sc}$	$V_{R_{TH}}$	$I_{R_{TH}}$	Original		Equivalent	
						$V_{R_L}$	$I_{R_L}$	$V_{R_L}$	$I_{R_L}$
<b>Calculated</b>									
<b>Simulated</b>									
<b>Measured</b>									
<b>Percent Error</b>									

Table 2.1 – Circuit #2 Data

**Part III – Thévenin Design Problem**

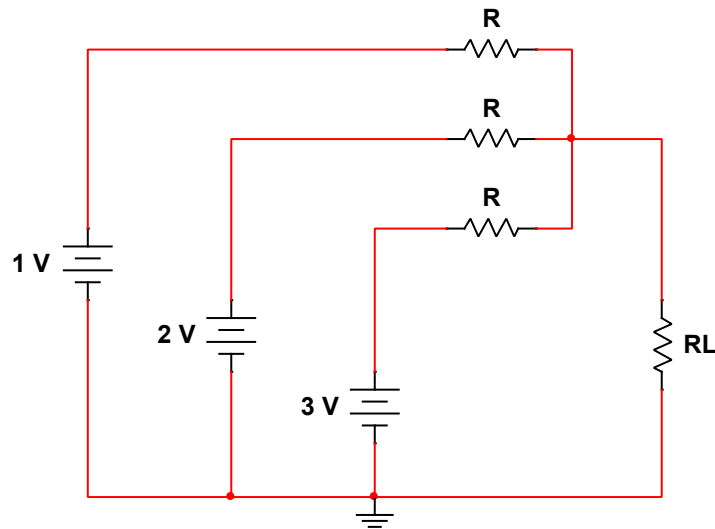


Figure 3.1 – Design Problem

1. **Determine** the resistances  $R$  and  $R_L$  such that the following specifications are met:
  - **Voltage across**  $R_L$  is equal to  $\frac{1}{2}V_{TH}$
  - **Maximum power** dissipated by  $R_L$  is 3mW

*Hint: Start by removing the load resistor and finding the Thévenin equivalent circuit as you have done for the previous circuits in this lab. You will need to find the value for  $R_L$  before solving for  $R$ . Also, note that all three resistors labeled  $R$  are the same value resistance.*

2. For your circuit with the calculated value of  $R$ , is there any other resistor that could be substituted in for  $R_L$  to increase the power dissipated by the load? **Explain.**

## **POST-LAB ANALYSIS**

Include answers to the following questions in the Analysis and Discussion section of your lab report.

1. When you attach the  $1\text{k}\Omega$  load resistor ( $R_L$ ) to any of the circuits in the lab, is the voltage across  $R_L$  equal to  $V_{TH}$ ? Is the current through  $R_L$  equal to  $I_{SC}$ ?
2. Is there any load resistor ( $R_L$ ) that you could attach to the circuit to achieve both  $V_{TH}$  and  $I_{SC}$  at the same time? Explain.
3. When you attach the Thévenin equivalent resistance ( $R_{TH}$ ) to any of the circuits in the lab, is there a relationship between  $V_{TH}$  and  $V_{R_{TH}}$ ? What about  $I_{SC}$  and  $I_{R_{TH}}$ ?

Include the following in the Conclusion of your lab report:

1. Discuss how Thévenin's Theorem helps you simplify the circuit analysis. For example, consider this idea when writing your conclusion: is it easier to use the Thevenin equivalent circuit to determine the voltage across and current through the load resistor ( $R_L$ ) or is it easier to use the original circuit?
2. What is the purpose of the Thévenin Equivalent circuit?