
THE GEORGE WASHINGTON UNIVERSITY

WASHINGTON, DC

SCHOOL OF ENGINEERING AND APPLIED SCIENCE
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING
ECE 2115: ENGINEERING ELECTRONICS LABORATORY

Experiment #7:
Designing and Measuring a Common-Emitter Amplifier

COMPONENTS

Type	Value	Symbol Name	Multisim Part	Description
Resistor	--- Ω	R_{B1}	Basic/Resistor	Determined in Prelab
Resistor	--- Ω	R_{B2}	Basic/Resistor	Determined in Prelab
Resistor	--- Ω	R_C	Basic/Resistor	Determined in Prelab
Resistor	--- Ω	R_E	Basic/Resistor	Determined in Prelab
Resistor	--- Ω	R_{E1}	Basic/Resistor	Determined in Prelab
Resistor	4k Ω	R_L	Basic/Resistor	---
Resistor	8 Ω	R_L	Basic/Resistor	---
Resistor	10k Ω	R_{test}	Basic/Resistor	---
Capacitor	--- F	C_{C1}, C_{C2}, C_{B1}	Basic/Capacitor	Determined in Prelab
Transistor	2N3904	Q_1	Transistors/BJT_NPN/2N3904	NPN BJT

Table 1 – Component List

OBJECTIVES

- To design a common-emitter amplifier to meet a set of specifications
- To simulate the designed common-emitter amplifier
- To build the designed common-emitter amplifier
- Measure voltage gain (A_V) with and without load in laboratory
- Measure R_{in} , R_{out} with and without load in laboratory

PRELAB

Part I – Generate Equipment List

1. Read through the lab manual and generate an equipment list.

Part II – Common-Emitter Amplifier Design

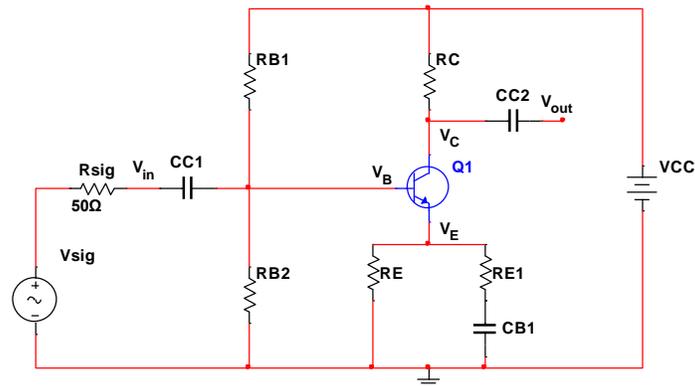


Figure P.1 – Common-Emitter Amplifier with Emitter Degeneration Parallel Resistor

1. Read the tutorial “**Designing a Common-Emitter Amplifier**” for help completing this prelab.
2. **Design a common-emitter amplifier** using a 2N3904 NPN BJT to meet the following specifications (hand in all calculations):
 - Quiescent Current (I_{CQ}) = 1mA
 - $V_{CC} = 20V$
 - A_{Vo} (unloaded) = -100 V/V
 - $R_{in} = 4k\Omega$
 - $R_L = 4k\Omega$
 - $V_{in} = 10mV @ 10kHz$
3. **Determine** the voltage gain (A_V) with load.
4. **Determine** the output impedance (R_{out}) **without** the load.
5. **Determine** the output impedance (R_{out}) **with** the load.

Part III – Common-Emitter Amplifier Simulation

1. **Build** the amplifier you have designed in Multisim. Use 50Ω for R_{sig} .
2. **Run a DC Operating Point Analysis** to determine the DC bias voltages and currents in the circuit.
 - a. **Show** the DC **voltages** and DC **currents** at every node.
 - b. **Verify** that the simulated DC values approximate your calculations.
3. **Run a Transient Analysis** to show five cycles of V_{in} (**not** V_{sig}) and V_{out} . Ensure that both voltages are plotted with their own y-axis as done in the previous lab.
 - a. Place labels at the peaks of V_{in} and V_{out} making sure to mark this at the **same point in time**.
 - b. **Determine** the small signal voltage gain of the amplifier (A_V) **with** and **without** the load. **Verify** that it approximates your calculations.
 - c. $R_{in}(AC) = V_{in} / I_{in}$. **Plot** and **measure** the input current I_{in} to determine $R_{in}(AC)$.
 - d. $R_{out}(AC) = V_{out} / I_{out}$. **Plot** and **measure** the output current I_{out} to determine $R_{out}(AC)$.
 - e. **Increase** V_{in} until V_{out} is distorted (looks like a clipped sine wave). For the maximum value of V_{in} , what is V_{out} ? Does it match the calculated max voltage swing from the IV curve for the 2N3904 transistor?

LAB

Part I – Bias Point Verification (DC Measurements)

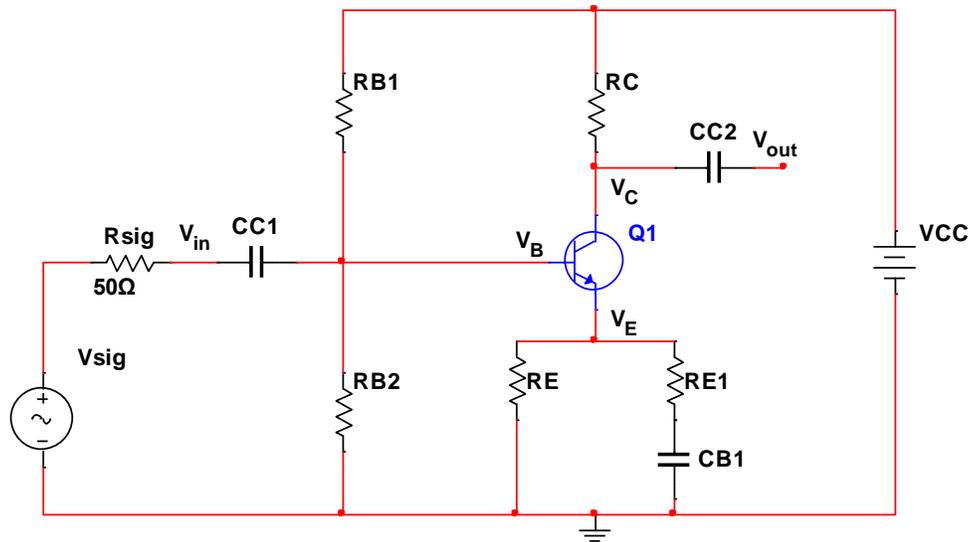
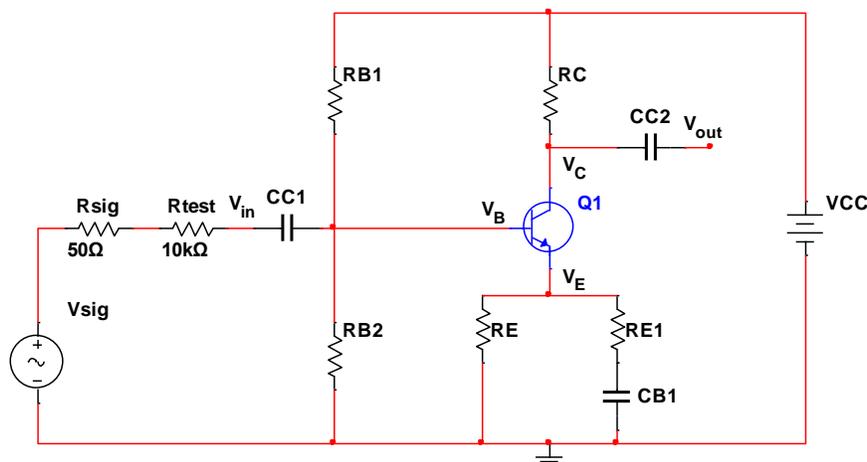


Figure 1.1 – Common-Emitter Amplifier with Emitter Degeneration Parallel Resistor

1. **Before building** the circuit in **Figure 1.1**, **measure** the exact resistances of **all** resistors using the DMM. **Record** these values.
2. **Build** the circuit in **Figure 1.1** using transistor 2N3904 and the resistor values found in the prelab.
3. **Before** attaching the function generator, oscilloscope, or the load:
 - a. **Measure** V_B , V_E , and V_C using the DMM.
 - b. From the measured voltages, **calculate** V_{BE} , V_{CE} , V_{CB} , I_B , I_E , I_C , and β .
4. **Place** all hand **calculated**, **simulated**, and **measured** values for I_B , I_E , I_C , V_B , V_E , V_C , V_{BE} , V_{CE} , V_{CB} , and β in a single table for analysis in your lab report.

Part II – Common-Emitter Amplifier Verification (Small-Signal Measurements)

1. **Apply** the 10mV, 10kHz input signal using the function generator with **no load** attached.
Note: The 10mV (20mV_{PP}) set on the function generator is “ v_{sig} ,” NOT “ v_{in} ” and the output impedance of the function generator is 50Ω (R_{sig}).
2. **Use** CH-1 of the oscilloscope to measure v_{in} .
 - a. You **CANNOT** use autose. Determine the proper period for the 10kHz signal.
 - b. **Ensure** CH-1 is set for **AC coupling**.
 - c. For CH-1, use the scope to set a **bandpass filter** to clear the noise from the circuit.
 - d. **Include** relevant measurements such as V_{max} on the waveform.
3. **Use** CH-2 of the oscilloscope to measure v_{out} .
 - a. You **CANNOT** use autose. Determine the proper period for the 10kHz signal.
 - b. **Ensure** CH-2 is set for **AC coupling**.
 - c. For CH-2, use the scope to set a **bandpass filter** to clear the noise from the circuit.
 - d. **Include** relevant measurements such as V_{max} on the waveform.
4. **Determine** A_{V_o} from the measured v_{out} , v_{in} .
5. **Measure** $R_{in} = V_{in} / I_{in}$.
 - a. Because the scope can only measure voltage (not current), we use the following technique to determine R_{in} :
 - i. You have previously recorded v_{in} .
 - ii. **Attach** a 10kΩ resistor between the function generator and your amplifier’s input. **Measure** the **voltage** across it.


 Figure 2.1 – Circuit with Inserted 10kΩ R_{test}

- iii. **Use** Ohm’s law to **calculate** the **current through** the 10kΩ resistor (I_{in}).
 - iv. Since the 10kΩ is in series with your amplifier, I_{in} is the same with or without the 10kΩ resistor.
 - v. **Calculate** $R_{in} = v_{in} / I_{in}$ (use the value for v_{in} recorded **before** the 10kΩ resistor).
6. **Increase** v_{in} until v_{out} **saturates** (clips). **Record** the value of v_{in} where saturation occurs.
7. **Attach** the 4kΩ load resistor and **measure** v_{out} (across the 4kΩ load). **Determine** $A_V(\text{loaded})$.
8. **Attach** an 8Ω load resistor and **measure** v_{out} (across the 8Ω load). **Determine** $A_V(8\Omega \text{ load})$.
 - a. **Calculate** the **current** (I_{out}) through this resistor.
9. **Attach** a load resistor that is the same size as R_C and **measure** v_{out} (across the load). **Determine** $A_V(R_C \Omega \text{ load})$.
10. **Calculate** $R_{out}(\text{unloaded}) = v_{out} / I_{out}$.
 - a. **Use** the value of v_{out} recorded when there was no load attached.
 - b. **Use** the value of I_{out} calculated when there was an 8Ω load attached.

POST-LAB ANALYSIS

1. **Include** all hand calculations in the final lab report.
2. For each part of the lab, **create tables** to compare your hand **calculated** data, **simulated** data, and **measured** data. If there are waveforms, include the waveforms from your prelab in your lab report to accurately compare them to the waveforms captured in lab.
3. **Calculate** percent error between hand **calculations**, **simulations**, and **measurements**.
4. **What** is the maximum output voltage swing of your amplifier?
 - a. Did it **match** your calculations?
5. Is the **input impedance** (R_{in}) of a common-emitter amplifier high or low? **Explain**.
6. Is the **output impedance** (R_{out}) of a common-emitter amplifier high or low? **Explain**.
7. **When** the amplifier is attached a **load comparable to R_C** , **what effect** does it have on the **gain**?
8. **When** the amplifier is attached a **small load**, **what effect** does it have on the **gain**? **Explain why** this occurs.
 - a. **What conclusion** can you draw about the type of load that a common-emitter amplifier can handle and still maintain gain?