

Tutorial #3:
Parametric Sweep Simulation of a BJT

INTRODUCTION

In this tutorial, we will discuss how to generate a typical I-V curve for a Bipolar Junction Transistor (BJT) in Multisim. To do this, a DC Sweep simulation will be combined with a parametric simulation.

BACKGROUND

Bipolar Junction Transistors

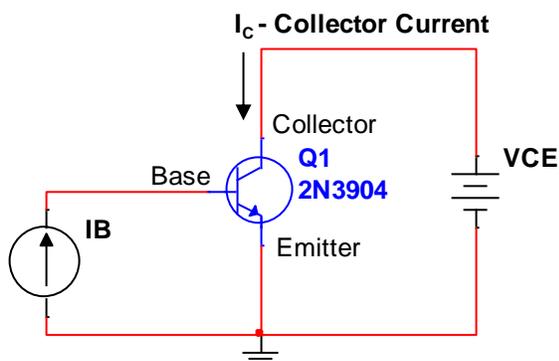


Figure 1 – BJT Test Circuit

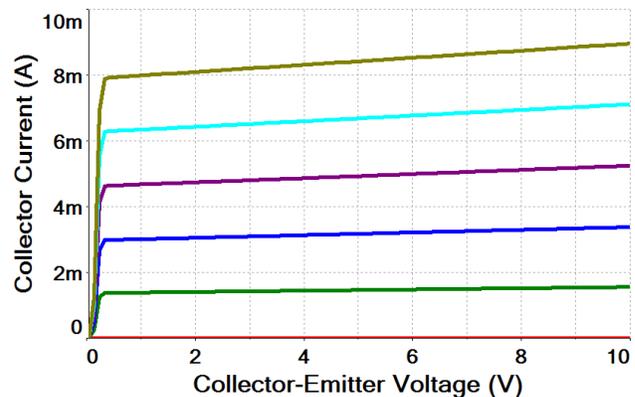


Figure 2 – BJT I-V Curve

A **Bipolar Junction Transistor** (BJT) is a three-terminal non-linear device. Current applied to the base of the transistor (I_B) controls the amount of current that will flow from the collector to the emitter (I_C). In theory, this is a “Current Controlled Current Source” (CCCS). I_B is the “control,” and the Collector-Emitter terminals act like those of a “current source,” where the current is I_C .

In order to “turn on” the BJT device, we follow a two-step process:

1. **Apply voltage** across the **Collector-Emitter** terminals (V_{CE}).
2. **Apply current** to the **base** terminal (I_B). Then current (I_C) will flow from the collector to the emitter, behaving as a current source.

To **characterize** the full range of operation of the device, we vary both V_{CE} and I_B to see the variation in I_C . The test circuit used to characterize a BJT device is shown in **Figure 1** above. The typical I-V curve that this test circuit will produce is shown in **Figure 2** above. This tutorial will explain how to produce the I-V curve using Multisim.

INSTRUCTIONS

Part I – Plotting a Single I-V Curve for a BJT

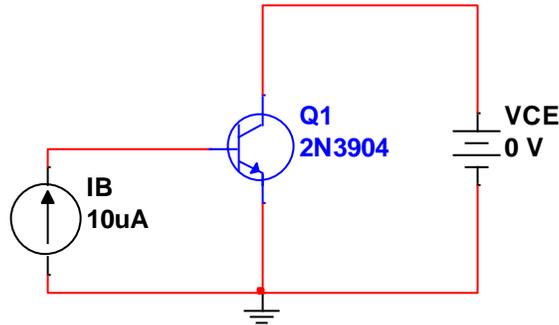


Figure 3 – BJT Characterization Circuit

1. **Build** the circuit in **Figure 3** in Multisim.
 - a. By default, the current source (I_{DC}) and voltage source (V_{DC}) will be named I1 and V1, respectively. **Rename** them to I_B and V_{CE} as you see in the schematic above.
 - b. Make certain that the current source is upwards so current goes “into” the base.
 - c. **Set $V_{CE} = 0V$ and $I_B = 10\mu A$.**
2. **Run a DC Sweep Analysis** to “sweep” V_{CE} from 0V to 10V while I_B pushes 10 μA into the base of the transistor and observe its effect on I_C .
 - a. **Set the Source** to be V_{CE}
 - b. **Start value:** 0V
 - c. **Stop value:** 10V
 - d. **Increment:** 0.1V
 - e. **Select I_C** of the transistor as the output
3. **Press Simulate** and you should see the following graph.

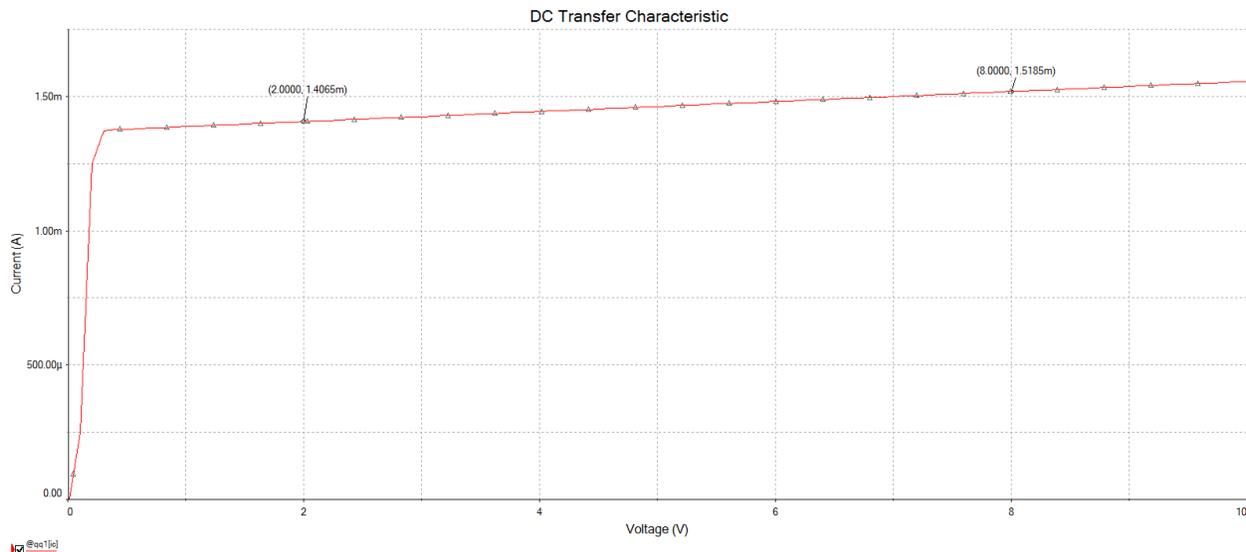


Figure 4 – I-V Curve for 2N3904 BJT ($I_B = 10\mu A$)

Note: This is a single I-V curve for a BJT. The x-axis is the “swept” variable (V_{CE}) and the y-axis is the collector current. From the markers on the graph, we see that for $I_B = 10\mu A$ and $V_{CE} = 2V$, $I_C = 1.4065mA$. When $I_B = 10\mu A$ and $V_{CE} = 8V$, $I_C = 1.5185mA$.

Part II – Plotting a Family of I-V Curves for a BJT

In the simulation above, I_B was fixed at $10\mu\text{A}$ while V_{CE} was swept. Now we would like to see how the BJT behaves if both V_{CE} and I_B are swept. This is known as a DC Sweep combined with a Parametric Sweep, often called a “**parametric simulation**.” In our case, I_B is the “parameter” we wish to vary while V_{CE} is swept.

1. Using the same circuit from the previous simulation, reopen the **DC Sweep Analysis** settings.
2. Click the box next to **Use source 2** to enable the second parameter I_B and enter these settings.
 - a. Set the **Source** to be I_B
 - b. **Start value:** 0A
 - c. **Stop value:** $50\mu\text{A}$ ($50\text{e-}6$)
 - d. **Increment:** $10\mu\text{A}$ ($10\text{e-}6$)
3. Run the simulation and the following graph should appear.

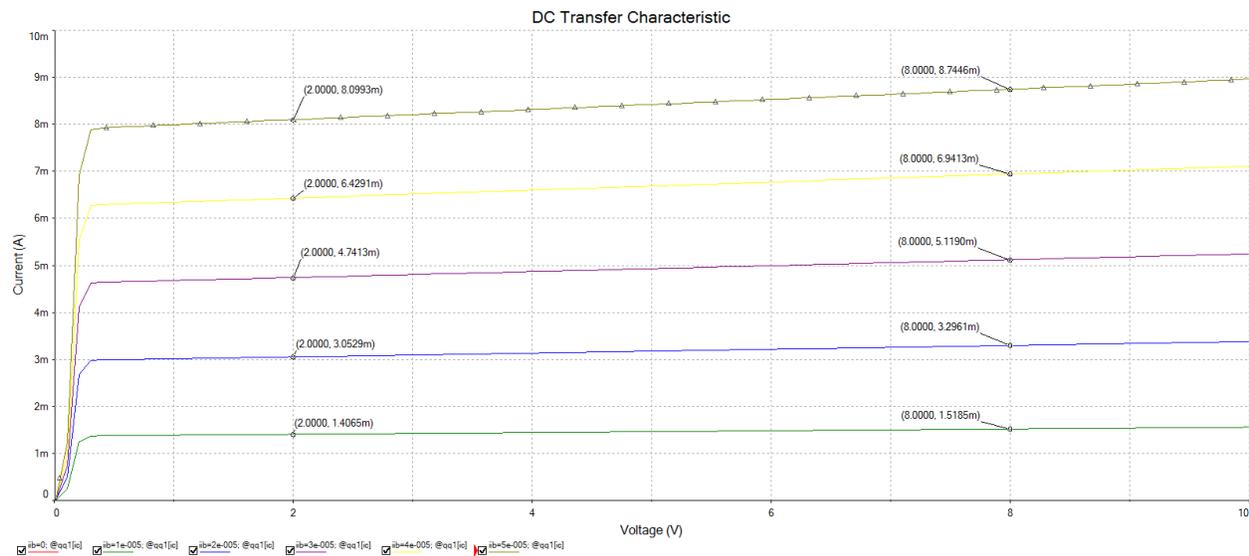


Figure 5 – Family of I-V Curves for 2N3904 BJT ($0\mu\text{A} \leq I_B \leq 50\mu\text{A}$)

Note: This is called a family of I-V curves for a BJT. The x-axis is still the “swept” variable (V_{CE}) and the y-axis is still the collector current. However, now there is one I-V curve for each value of I_B that we specified: $0\mu\text{A}$, $10\mu\text{A}$, $20\mu\text{A}$, $30\mu\text{A}$, $40\mu\text{A}$, and $50\mu\text{A}$.

From the markers on the blue graph, we can interpret the following:

- When $I_B = 10\mu\text{A}$ and $V_{CE} = 2\text{V}$, $I_C = 1.4065\text{mA}$.
- When $I_B = 10\mu\text{A}$ and $V_{CE} = 8\text{V}$, $I_C = 1.5185\text{mA}$.

From the markers on the top green graph, we can interpret the following:

- When $I_B = 50\mu\text{A}$ and $V_{CE} = 2\text{V}$, $I_C = 8.0993\text{mA}$.
- When $I_B = 50\mu\text{A}$ and $V_{CE} = 8\text{V}$, $I_C = 8.7446\text{mA}$.

What is incredibly important to take away from the second graph is the effect of I_B on the transistor. Notice that I_C (collector current) is small ($\sim 1.5\text{mA}$) when I_B is small ($10\mu\text{A}$) for the given values of V_{CE} . But when we increase I_B to $50\mu\text{A}$, I_C is much, much higher ($\sim 8.5\text{mA}$) for the same values of V_{CE} ! In effect, I_B has “controlled” the value of I_C , showing how this device behaves as a “current controlled current source.” It can be confusing, but if you look at the graph and ask questions in lab, this will be clearer.