

THE GEORGE WASHINGTON UNIVERSITY

WASHINGTON, DC

School of Engineering and Applied Science
Department of Electrical and Computer Engineering
ECE 20 - LAB

Experiment # 12

MOSFET Amplifiers testing and designing

Equipment:

You must make up a complete equipment list and have your instructor review it before you start.

Objectives:

- To verify the operating point for a MOSFET biasing network
- To verify the small signal performance for a given CSC amplifier: R_{IN} , R_{OUT} , A_v , A_i , maximum input amplitude without distortion $V_{in\ max}$, etc.
- To verify the small signal performance for a given CDC amplifier: R_{IN} , R_{OUT} , A_v , A_i , maximum input amplitude without distortion $V_{in\ max}$, etc.
- To establish the relationship between the voltage gain and the load

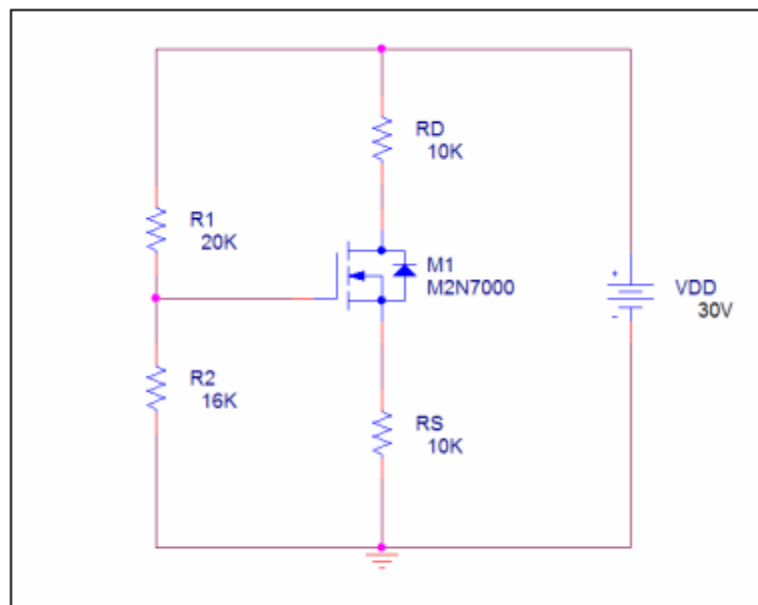


Figure # 1 – DC Biased MOSFET

1.- (HW) Analysis

- a. Analyze the circuit shown in Figure # 1 (use nominal values) and find VGG, VG, VS, VD, and ID
(assume $V_{DD} = 30$ Volts DC, $K = 64$ mAmp/Volt², $V_{th} = 1.73$ V).
note: $K = k_n'$ (W/L)
- b. Assemble this circuit on SPICE
 - For M1, use Part: M2N7000 (**note:** the student edition doesn't include this part)
 - Analysis Type: Bias Type
 - Show the DC Node Voltages and Currents, to verify your calculations

2.- Verification

- a. Build and fully test the circuit shown in Figure #1. Measure VG, VS, VD, and ID using the DMM.

3.- (HW) Analysis

Figure #1 can be configured as a CSC or CDC Amplifier. The DC Bias voltages and current remain the same as in Part 1 of this lab. Using the DC Bias Voltages & Currents that you have found, analyze the two different Amplifier Configurations below:

1. Refer to Figure #2 which shows the CSC configuration of the amplifier:
 - a. Find R_{OUT} , R_{IN} , A_{vo} , A_v (set $R_L=R_{OUT}$) and A_i (set $R_L=R_{OUT}$).
 - b. Also, find the maximum input voltage ($V_{in\ max}$) that the amplifier can accept before the output distorts (loaded and unloaded).
2. Create Figure #3, which connects Figure #1 in the CDC configuration.
 - a. Use a “shorting capacitor” C_S , as was done in Figure #2, to short R_D .
 - b. Find R_{OUT} , R_{IN} , A_{vo} , A_v ($R_L=R_{OUT}$) and A_i ($R_L=R_{OUT}$).
 - c. Also, find the maximum input voltage ($V_{in\ max}$) that the amplifier can accept before the output distorts (loaded and unloaded).

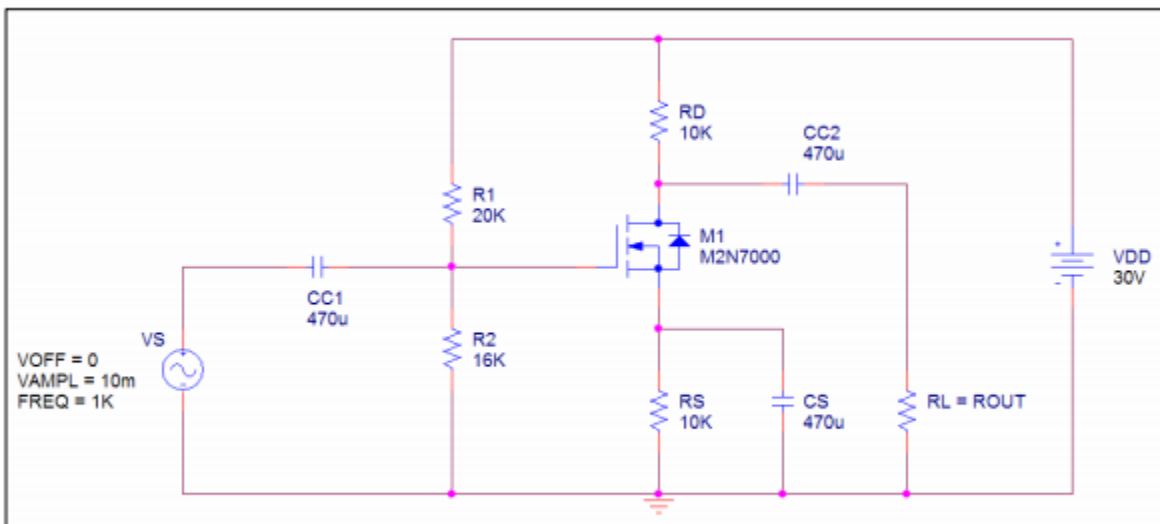


Figure #2 – MOSFET configured as a CSC (Common Source Configuration) Amplifier

(Your Image Here)

Figure #3 – (HW) Your design for MOSFET configured as a CDC (Common Drain Configuration) Amp is called Figure 3

4.- Verification

Build and fully test the circuits shown in Figure #2 & Figure #3. Applying a sinusoidal signal, V_s (using the function generator), such that the small signal approximation holds (use $V_s=10\text{mV}$ at 1KHz), measure:

1. Build the CSC Amplifier from Figure #2:
 - a. Voltage gain A_{vo} the assembled circuit for the *unloaded* case (no CC_2 or RL). Repeat and find A_v with a load of $RL=R_{OUT}$. Use the oscilloscope to compare V_S to V_{out}
 - b. Find R_{IN} (input impedance) and R_{OUT} (output impedance) of the assembled circuit.
 - c. Find the maximum input voltage that the amplifier can accept before the output distorts (loaded case $RL = R_{OUT}$). Plot the output signal and the corresponding input.
 - d. Determine the phase relationship between the input and output voltages.
 - e. Compare the measured results to your analysis calculations.

2. Build the CDC Amplifier from Figure #3. (*note: This portion may be skipped to save lab time – this is at the discretion of your GTA*):
 - a. Voltage gain A_{vo} the assembled circuit for the *unloaded* case (no CC_2 or RL). Repeat and find A_v with a load of $RL=R_{OUT}$. Use the oscilloscope to compare V_S to V_{out} .
 - b. Find R_{IN} (input impedance) and R_{OUT} (output impedance) of the assembled circuit.
 - c. Find the maximum input voltage that the amplifier can accept before the output distorts (loaded case $RL = R_{OUT}$). Plot the output signal and the corresponding input.
 - d. Determine the phase relationship between the input and output voltages.
 - e. Compare the measured results to your analysis calculations.

Hint: Connect a large capacitor between V_{CC} and ground in order to remove all the noise from the source. The noise is amplified and mixes with the output. You may also apply a bandpass filter to channel 1 of the digital oscilloscope to reduce the noise.

5.- (HW) Design of Common Source

Design a Common Source voltage amplifier (with shorting capacitor) similar to the one shown in Figure # 1. Use SPICE to verify that all the specifications have been achieved.

Design Specifications of the Amplifier

- **VDD = 18 V DC**
- **RL = 5 kΩ**
- **|Av| ~ 30 (with RL). |Av| > 30 is even better!**
- **750 kΩ < RIN < 10 kΩ -- R1 and R2 should be in the kΩ range**
- **Vin max (before distortion) ≥ 60 mVpeak (when loaded with RL = 5 kΩ)**
- **Maximum Power must occur when loaded with RL = 5 kΩ ± 5%**

(Recall maximum power transfer theorem related to Thevenin's theorem)

Assumptions:

- **K = 64 mAmp/Volt** *note:* $K = k_n' (W/L)$
 - **Vth = 1.73 V**
 - **Vs = Vds = 1/3(VDD)** ("Rule of Thumb" from textbook)
 - **RD = RS**, and that $r_o \gg RD$ and $r_o \gg RS$
- Find R1, R2, RD & RS, as well as all voltages/currents. Show all design calculations.
 - Compare the SPICE results to your design calculations and specifications and explain any and all differences.

6.- Assembly, Test and Verification of Specifications

Build and test your design. Measure and verify that your design meets all the given specifications.

- a. Measure VG, VS, VD, and ID with no input.
- b. Measure Avo, Av (RL = at max power transfer), Rin (input impedance) and Rout (output impedance) of the assembled circuit.
- c. Find the maximum input voltage that the amplifier can accept before the output distorts.
- d. Measure the phase relationship between the input and output voltages.

7.- Conclusion

- a. Considering that these amplifiers are quite typical, what can you say about R_{IN} , R_{OUT} , and the A_v for the CSC and CDC amplifiers?
- b. Based on your observation, what are the primary differences between BJT and MOSFET Amplifiers?
- c. Compare the measured results to your design calculations and specifications. Explain any and all differences!