
THE GEORGE WASHINGTON UNIVERSITY

WASHINGTON, DC

SCHOOL OF ENGINEERING AND APPLIED SCIENCE
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING
ECE 2115: ENGINEERING ELECTRONICS LABORATORY

Experiment #5:
Characterization of an NPN Bipolar Junction Transistor (BJT)

COMPONENTS

<i>Type</i>	<i>Value</i>	<i>Symbol Name</i>	<i>Multisim Part</i>	<i>Description</i>
Resistor	1k Ω	R _B	Basic/Resistor	---
Resistor	100k Ω	R _C	Basic/Resistor	---
Transistor	2N3904	Q ₁	Transistors/BJT_NPN/2N3904	NPN BJT

Table 1 – Component List

OBJECTIVES

- To characterize a BJT using a DC power supply and DMM
- To compare measured characterization results to manufacturer specifications

PRELAB

Part I – Generate Equipment List

1. Read through the lab manual and generate an equipment list.

Part II – Parametric Sweep Simulation of a BJT

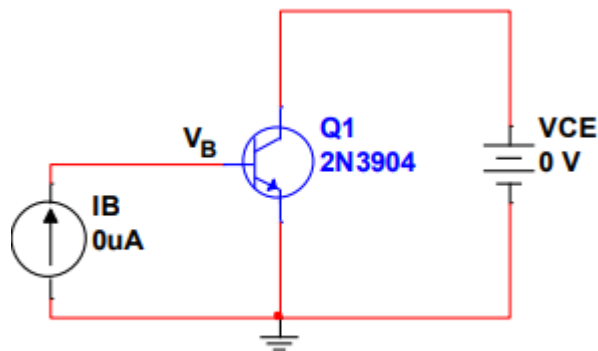


Figure P.1 – BJT Test Circuit

1. **Build** and **simulate** the circuit in **Figure P.1** using Multisim.
 - a. Use the “**Parametric Sweep Simulation of a BJT**” tutorial on the lab website to generate an I-V curve (I_C vs. V_{CE}) for the 2N3904 BJT.
 - b. **Sweep** V_{CE} from **0V** to **10V** in **0.2V** increments.
 - c. **Sweep** I_B from **10 μ A** to **50 μ A** in **20 μ A** increments.
 - d. **Plot** the collector current to generate three different I-V curves.
 - e. **Place** markers at $V_{CE} = 2V$ on each curve.
 - f. **Record** the values for V_{CE} , I_C , and I_B from the markers in **Table P.1**.
 - g. **Re-run** the simulation, plotting the voltage at node V_B instead of the collector current and again place markers at $V_{CE} = 2V$.
 - h. **Record** the values for V_{BE} from the markers in **Table P.1**.

I_B	Value	Calculated	Simulated	Measured
10μA	I_B			
	V_{CE}			
	I_C			
	V_{BE}			
	β			
30μA	I_B			
	V_{CE}			
	I_C			
	V_{BE}			
	β			
50μA	I_B			
	V_{CE}			
	I_C			
	V_{BE}			
	β			

Table P.1 – BJT Values

Part III – BJT Calculations

1. Use Equation P.1 to calculate I_C and record the values in the calculated section of **Table P.1**.
 - a. Calculate I_C for each value of V_{BE} collected in the simulations in **Part II**.
 - b. Assume $I_S = 6.734\text{fA}$ and the typical value for $V_T = 26\text{mV}$ (thermal voltage).
 - c. Calculate the value of the DC current gain ($\beta = I_C / I_B$) for each value of I_B in **Table P.1**.

$$I_C \cong I_S \left(e^{\frac{V_{BE}}{V_T}} \right)$$

 Equation P.1 – Collector Current of NPN BJT in the Active Region of Operation
 (Assumes $V_A \gg V_{CE}$ and $n = 1$)

Part IV – Specification Sheet Values

1. In the simulation above, we have swept V_{CE} from 0V to 10V and I_B from 10 μ A to 50 μ A. However, the 2N3904 BJT can handle a significantly higher set of values.
 - a. From the specification sheet for the 2N3904 BJT, gather the following specifications:

<i>Parameter</i>	<i>Value</i>
Maximum Collector-Emitter Voltage (V_{CEO})	
Maximum Emitter-Base Voltage (V_{EBO})	
Maximum Continuous Collector Current (I_C)	
Maximum Collector-Base Voltage (V_{CBO})	
Maximum DC Current Gain (β or h_{FE})	
Base-Emitter ON Voltage (V_{BE}) when $V_{CE}=5V$ and $I_C=10mA$ at room temperature	

Table P.2 – 2N3904 BJT Spec Sheet Values

LAB

Part I – Transistor Characterization Using a Test Circuit

In this part of the lab, you will generate only three I-V curves (I_C vs. V_{CE}) as you did in the prelab. I_B will be the parameter whose value will step from $10\mu A$ to $50\mu A$ in $20\mu A$ steps.

In the prelab, you generated an I-V curve for the 2N3904 transistor using the schematic in **Figure P.1**. You were able to generate base current I_B in the range of $0\mu A$ to $50\mu A$. In the lab, the power supply can behave as a current source, but it **cannot** produce a current as small as $50\mu A$. To create the same family of I-V curves in the lab, we must use the circuit in **Figure 2.1**. The voltage source combined with the $100k\Omega$ resistor at the base will behave as the $0\mu A$ to $50\mu A$ current source from **Figure P.1**.

The data collected during this part of the lab is to be recorded under the **Measured** column of **Table**


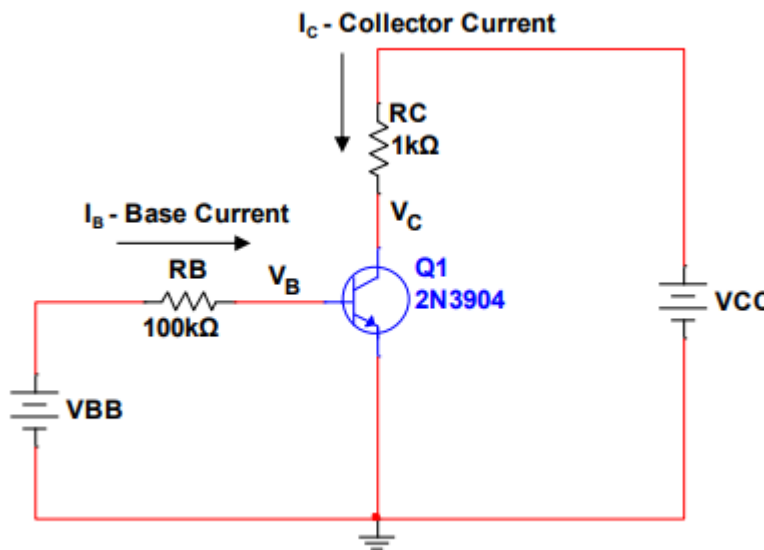


Figure 2.1 – BJT Test Circuit to Generate Family of I-V Curves

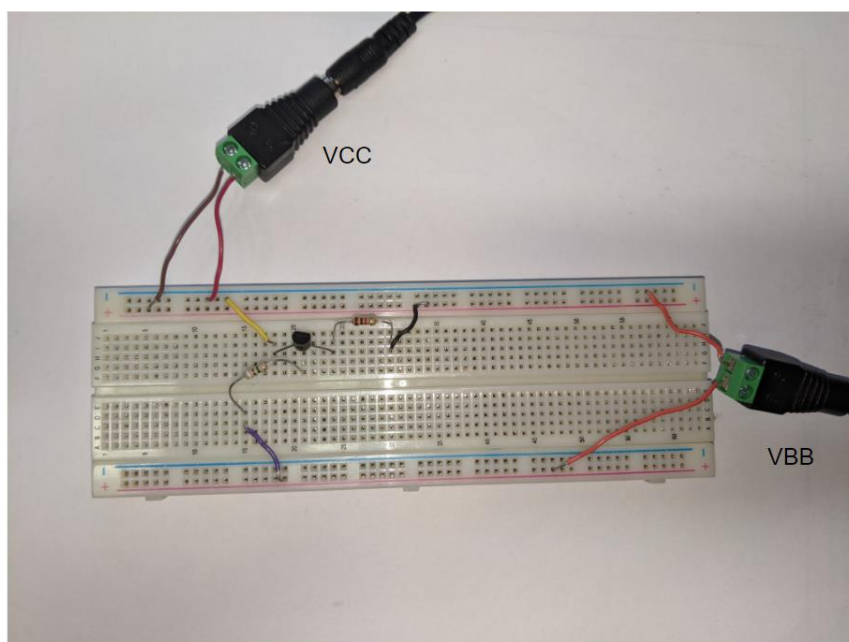

1. **Measure** the $I_B = 10\mu\text{A}$ curve.
 - a. **Build** the circuit depicted in **Figure 2.1** using the 2N3904 BJT.
 - b. **Measure** the exact resistances of R_B and R_C using the DMM and record these values.
 - c. **Use** a DMM to measure the voltage at node V_B in the circuit. This is V_{BE} .
 - d. **Use** a DMM to measure the voltage at node V_C in the circuit. This is V_{CE} .
 - e. **Adjust** V_{CC} until V_{CE} equals 2V.
 - f. **Adjust** V_{BB} until V_{BE} equals the value found in the prelab when $I_B = 10\mu\text{A}$ and $V_{CE} = 2\text{V}$.
 - g. **Readjust** V_{CC} until V_{CE} equals 0V.
 - h. **Record** V_{CC} , V_{CE} , V_{BB} , and V_{BE} in **Table P.1**.
 - i. **Calculate** the voltage across R_B to **calculate** and **record** the current I_B in **Table P.1**.
 - j. **Calculate** the voltage across R_C to **calculate** and **record** the current I_C in **Table P.1**.
 - k. **Adjust** V_{CE} from 0V to 2V in 0.2V increments, repeating steps h-j at each step.
 - l. **Adjust** V_{CE} from 2V to 10V in 1V increments, repeating steps h-j at each step.
 - m. **Calculate** β for each recorded value of I_C and I_B .

Note: Remember, you can do voltages from -5 to 5 Volts using the AD2. If you need voltages higher than this, you will need to use the 3-24V power sources.

2. **Measure** the $I_B = 30\mu\text{A}$ curve.
 - a. **Repeat** steps a-m above, but in step f, adjust V_{BB} until $I_B = 30\mu\text{A}$. You will need to calculate the current I_B from the voltage across R_B .
3. **Measure** the $I_B = 50\mu\text{A}$ curve.
 - a. **Repeat** steps a-m above, but in step f, adjust V_{BB} until $I_B = 50\mu\text{A}$. You will need to calculate the current I_B from the voltage across R_B .

POST-LAB ANALYSIS

1. **Plot** a family of I-V curves for the **calculated** and **measured** data collected in **Table P.1**.
2. **Compare** the **Calculated**, **Simulated**, and **Measured** (DMM) results via graphs (overlying them where possible) and percentage error in all cases.