

---

---

# THE GEORGE WASHINGTON UNIVERSITY

---

---

WASHINGTON, DC

SCHOOL OF ENGINEERING AND APPLIED SCIENCE  
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING  
ECE 2115: ENGINEERING ELECTRONICS LABORATORY

Experiment #7:  
*Designing and Measuring a Common-Emitter Amplifier*

## COMPONENTS

Type	Value	Symbol Name	Multisim Part	Description
Resistor	---	$R_{B1}$	Basic/Resistor	Determined in Prelab
Resistor	---	$R_{B2}$	Basic/Resistor	Determined in Prelab
Resistor	---	$R_C$	Basic/Resistor	Determined in Prelab
Resistor	---	$R_E$	Basic/Resistor	Determined in Prelab
Resistor	---	$R_{E1}$	Basic/Resistor	Determined in Prelab
Resistor	4k $\Omega$	$R_L$	Basic/Resistor	---
Resistor	8 $\Omega$	$R_L$	Basic/Resistor	---
Resistor	10k $\Omega$	$R_{test}$	Basic/Resistor	---
Capacitor	---	$C_{C1}, C_{C2}, C_{B1}$	Basic/Capacitor	Determined in Prelab
Transistor	2N3904	$Q_1$	Transistors/BJT_NPN/2N3904	NPN BJT

Table 1 – Component List

## OBJECTIVES

- To design a common-emitter amplifier to meet a set of specifications
- To simulate the designed common-emitter amplifier
- To build the designed common-emitter amplifier
- Measure voltage gain ( $A_V$ ) with and without load in laboratory
- Measure  $R_{in}$ ,  $R_{out}$  with and without load in laboratory

## PRELAB

### Part I – Generate Equipment List

1. Read through the lab manual and generate an equipment list.

### Part II – Common-Emitter Amplifier Design

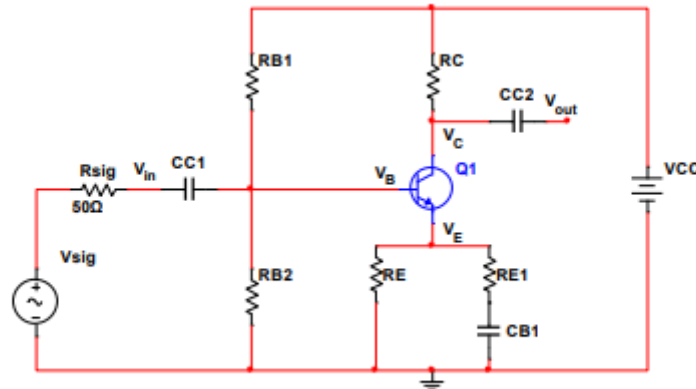


Figure P.1 – Common-Emitter Amplifier with Emitter Degeneration Parallel Resistor


1. Read the tutorial “Designing a Common-Emitter Amplifier” for help completing this prelab.
2. Design a common-emitter amplifier using a 2N3904 NPN BJT to meet the following specifications (hand in all calculations):
  - Quiescent Current ( $I_{CQ}$ ) = 1 mA
  - $V_{CC} = 20V$
  - $A_{V_o}$  (unloaded) = -100 V/V
  - $R_{in} = 4k\Omega$
  - $R_L = 4k\Omega$
  - $V_{in} = 10mV @ 10kHz$
3. Determine the voltage gain ( $A_v$ ) with load.
4. Determine the output impedance ( $R_{out}$ ) without the load.
5. Determine the output impedance ( $R_{out}$ ) with the load.

### Part III – Common-Emitter Amplifier Simulation

1. Build the amplifier you have designed in Multisim. Use 50Ω for  $R_{sig}$ .
2. Run a DC Operating Point Analysis to determine the DC bias voltages and currents in the circuit.
  - a. Show the DC voltages and DC currents at every node.
  - b. Verify that the simulated DC values approximate your calculations.
3. Run a Transient Analysis to show five cycles of  $V_{in}$  (not  $V_{sig}$ ) and  $V_{out}$ . Ensure that both voltages are plotted with their own y-axis as done in the previous lab.
  - a. Place labels at the peaks of  $V_{in}$  and  $V_{out}$  making sure to mark this at the same point in time.
  - b. Determine the small signal voltage gain of the amplifier ( $A_v$ ) with and without the load. Verify that it approximates your calculations.
  - c.  $R_{in}(AC) = V_{in} / I_{in}$ . Plot and measure the input current  $I_{in}$  to determine  $R_{in}(AC)$ .
  - d.  $R_{out}(AC) = V_{out} / I_{out}$ . Plot and measure the output current  $I_{out}$  to determine  $R_{out}(AC)$ .
  - e. Increase  $V_{in}$  until  $V_{out}$  is distorted (looks like a clipped sine wave). For the maximum value of  $V_{in}$ , what is  $V_{out}$ ? Does it match the calculated max voltage swing from the IV curve for the 2N3904 transistor?

**LAB**

**Part I – Bias Point Verification (DC Measurements)**

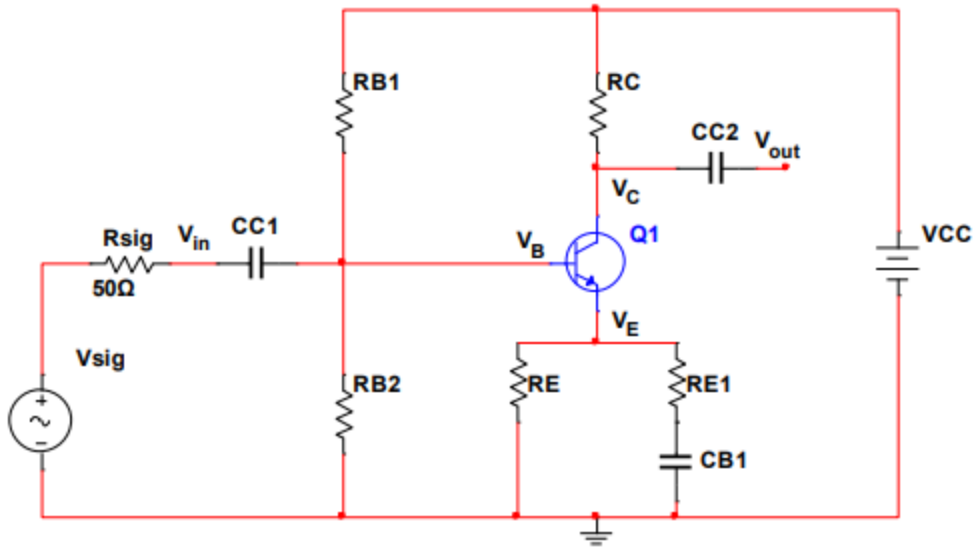

**Figure 1.1 – Common-Emitter Amplifier with Emitter Degeneration Parallel Resistor**

1. **Before building** the circuit in **Figure 1.1**, **measure** the exact resistances of **all** resistors using the DMM. **Record** these values.
2. **Build** the circuit in **Figure 1.1** using transistor 2N3904 and the resistor values found in the prelab.
3. **Before** attaching the function generator (Wavegen), oscilloscope, or the load:
  - a. **Measure**  $V_B$ ,  $V_E$ , and  $V_C$  using the DMM.
  - b. From the measured voltages, **calculate**  $V_{BE}$ ,  $V_{CE}$ ,  $V_{CB}$ ,  $I_B$ ,  $I_E$ ,  $I_C$ , and  $\beta$ .
4. **Place** all hand **calculated**, **simulated**, and **measured** values for  $I_B$ ,  $I_E$ ,  $I_C$ ,  $V_B$ ,  $V_E$ ,  $V_C$ ,  $V_{BE}$ ,  $V_{CE}$ ,  $V_{CB}$ , and  $\beta$  in a single table for analysis in your lab report.

**Part II – Common-Emitter Amplifier Verification (Small-Signal Measurements)**

1. **Apply** the 10mV, 10kHz input signal using the function generator (Wavegen) with **no load** attached.
 

**Note:** The 10mV (20mV<sub>PP</sub>) set on the function generator (Wavegen) is “v<sub>sig</sub>,” NOT “v<sub>in</sub>” and the output impedance of the function generator (Wavegen) is 50Ω (R<sub>sig</sub>).
2. **Use** CH-1 of the oscilloscope to measure v<sub>in</sub>.
  - a. You **CANNOT** use autoset. Determine the proper period for the 10kHz signal.
  - b. **Ensure** CH-1 is set for **Peak to Peak to get the gain. Remember,**

$$\frac{\text{Max Output}}{\text{Max Input}} = \frac{V_{\text{peak to peak output}}}{V_{\text{peak to peak input}}}$$
  - c. For If you are experiencing any noise, add a shunt capacitor
  - d. **Include** relevant measurements such as V<sub>max</sub> on the waveform.
3. **Use** CH-2 of the oscilloscope to measure v<sub>out</sub>.
  - a. You **CANNOT** use autoset. Determine the proper period for the 10kHz signal.
  - b. **Ensure** CH-2 is set for **Peak to Peak to get the gain.**
  - c. If you are experiencing any noise, add a shunt capacitor
  - d. **Include** relevant measurements such as V<sub>max</sub> on the waveform.
4. **Determine** A<sub>v0</sub> from the measured v<sub>out</sub>, v<sub>in</sub>.
5. **Measure** R<sub>in</sub> = V<sub>in</sub> / I<sub>in</sub>.
  - a. Because the scope can only measure voltage (not current), we use the following technique to determine R<sub>in</sub>:
    - i. You have previously recorded v<sub>in</sub>.
    - ii. **Attach** a 10kΩ resistor between the function generator (Wavegen) and your amplifier’s input. Measure the voltage across it.

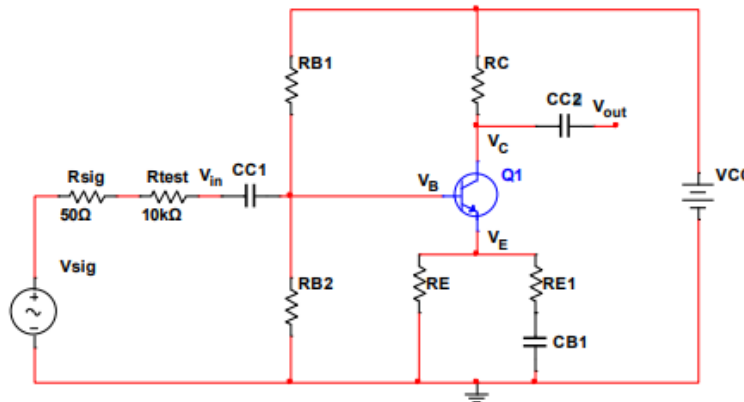


Figure 2.1 – Circuit with Inserted 10kΩ R<sub>test</sub>

- iii. **Use** Ohm’s law to **calculate** the **current through** the 10kΩ resistor (I<sub>in</sub>). iv. Since the 10kΩ is in series with your amplifier, I<sub>in</sub> is the same with or without the 10kΩ resistor.
    - v. **Calculate** R<sub>in</sub> = v<sub>in</sub> / I<sub>in</sub> (use the value for v<sub>in</sub> recorded **before** the 10kΩ resistor).
6. **Increase** v<sub>in</sub> until v<sub>out</sub> **saturates** (clips). **Record** the value of v<sub>in</sub> where saturation occurs.
7. **Attach** the 4kΩ load resistor and **measure** v<sub>out</sub> (across the 4kΩ load). **Determine** A<sub>v</sub> (loaded).
8. **Attach** an 8Ω load resistor and **measure** v<sub>out</sub> (across the 8Ω load). **Determine** A<sub>v</sub> (8Ω load).
  - a. **Calculate** the **current** (I<sub>out</sub>) through this resistor.
9. **Attach** a load resistor that is the same size as R<sub>c</sub> and **measure** v<sub>out</sub> (across the load). **Determine** A<sub>v</sub> (R<sub>c</sub> Ω load).
10. **Calculate** R<sub>out</sub>(unloaded) = v<sub>out</sub> / I<sub>out</sub>.
  - a. **Use** the value of v<sub>out</sub> recorded when there was no load attached.
  - b. **Use** the value of I<sub>out</sub> calculated when there was an 8Ω load attached.

### **POST-LAB ANALYSIS**

1. **Include** all hand calculations in the final lab report.
2. For each part of the lab, **create tables** to compare your hand **calculated** data, **simulated** data, and **measured** data. If there are waveforms, include the waveforms from your prelab in your lab report to accurately compare them to the waveforms captured in lab.
3. **Calculate** percent error between hand **calculations**, **simulations**, and **measurements**.
4. **What** is the maximum output voltage swing of your amplifier?
  - a. Did it **match** your calculations?
5. Is the **input impedance** ( $R_{in}$ ) of a common-emitter amplifier high or low? **Explain**.
6. Is the **output impedance** ( $R_{out}$ ) of a common-emitter amplifier high or low? **Explain**.
7. **When** the amplifier is attached a **load comparable to  $R_c$** , **what effect** does it have on the **gain**?
8. **When** the amplifier is attached a **small load**, **what effect** does it have on the **gain**? **Explain why** this occurs.
  - a. **What conclusion** can you draw about the type of load that a common-emitter amplifier can handle and still maintain gain?